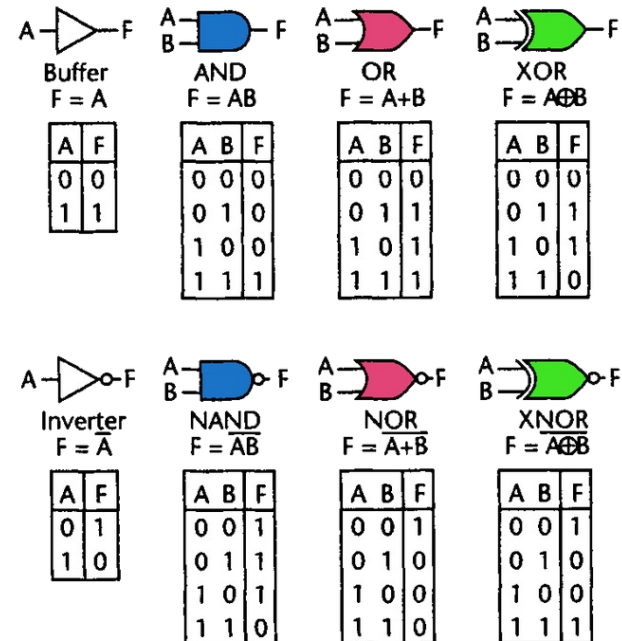


EE2000 Logic Circuit Design


Recap Lecture 1 – Logic Function and Boolean Algebra




Outline

- 1.1 Basic Logic Gates
- 1.2 Logic Circuit and Boolean Expression
- 1.3 Sum of Products vs Product of Sums and Canonical Form
- 1.4 Simplification using Boolean Algebra

Logic Gate


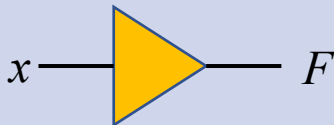
Logic Name	Circuit Diagram	Truth Table	Boolean Function						
Buffer: Output (F) follows the same logic state as the Input (x)		<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1	$F(x) = x$ $F = x$
x	F								
0	0								
1	1								
 
$$F(x, y) = x \cdot y + \overline{x} \cdot \overline{y}$$





- Function (F): Operation
- Variable: Inputs (x, y)
- Complement: Inversion (\bar{x}, \bar{y})
- Literal: Each appearance of a variable or its complement (4)
- Product term: One or more literals connected by \cdot operator (2)

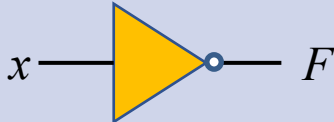
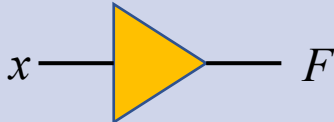
NOT Gate

Logic Name	Circuit Diagram	Truth Table	Boolean Function						
NOT gate (Inverter): Output (F) has opposite logic state of the Input (x)		<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0	$F = \bar{x}$ $F = x'$
x	F								
0	1								
1	0								
Logic Name	Circuit Diagram	Truth Table	Boolean Function						
Buffer: Output (F) follows the same logic state as the Input (x)		<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1	$F(x) = x$ $F = x$
x	F								
0	0								
1	1								



AND & NAND Gates

Logic Name	Circuit Diagram	Truth Table	Boolean Function															
AND gate: Output (F) is 1 only when all inputs are 1		<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1	$F = x \cdot y$ $F = xy$
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
NAND gate: Output (F) is 0 only when all inputs are 1		<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0	$F = \overline{x \cdot y}$ $F = \overline{xy}$
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																

OR & NOR Gates

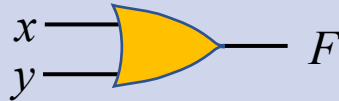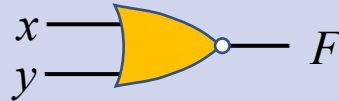Logic Name	Circuit Diagram	Truth Table	Boolean Function															
OR gate: Output (F) is 1 when either or all inputs are 1		<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1	$F = x + y$
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOR gate: Output (F) is 1 only when all inputs are 0		<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0	$F = \overline{x + y}$
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																

XOR & XNOR Gates

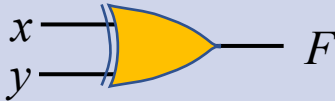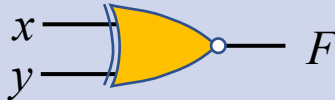Logic Name	Circuit Diagram	Truth Table	Boolean Function															
XOR gate: Output (F) is 1 only when one of the input is 1		<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0	$F = x \oplus y$
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
XNOR gate: Output (F) is 1 only when all inputs are 0 or 1		<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1	$F = \overline{x \oplus y}$ $F = x \otimes y$
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																


1.3 Sum of Products vs Product of Sums, Canonical Form

- Product terms: One or more literals connected by AND operator.

$$x, xy', xyz', y'z'$$

- Standard product terms: A product term that includes each variable of the problem, either uncomplemented or complemented.

$$xyz, xy'z', x'yz', x'y'z'$$

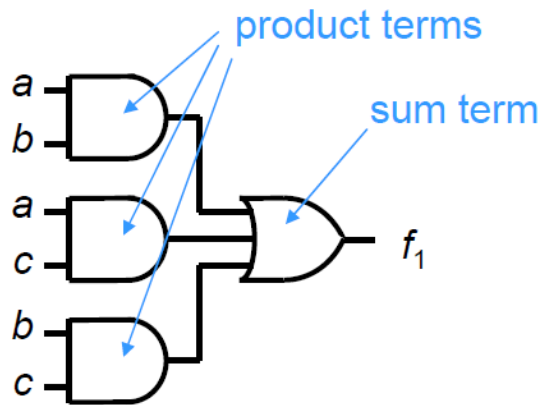

$$f_1(a, b, c) = ab + ac + bc$$

- Sum of Products (SOP): A group of AND gates followed by a single OR gate.

$$xy + yz + x'z + z' \quad 4 \text{ product terms}$$

$$xy + yz + x'z \quad 3 \text{ product terms}$$

$$xy + yz \quad 2 \text{ product terms}$$

$$xy \quad 1 \text{ product term}$$

Canonical (Standard) Form in SOP

Inputs			Minterms		Output
x	y	z	Term	Designation	$f(x, y, z)$
0	0	0	$x'y'z'$	m_0	1
0	0	1	$x'y'z$	m_1	0
0	1	0	$x'yz'$	m_2	1
0	1	1	$x'yz$	m_3	0
1	0	0	$xy'z'$	m_4	1
1	0	1	$xy'z$	m_5	1
1	1	0	xyz'	m_6	0
1	1	1	xyz	m_7	0

- Minterms: Standard product terms. Uncomplement = 1; Complement = 0.
- Canonical Sum (Sum of standard product terms): Sum of products expression with minterms only when output is 1


$$\begin{aligned}
 f(x, y, z) &= x'y'z' + x'yz' \\
 &\quad + xy'z' + xy'z \\
 &= m_0 + m_2 + m_4 + m_5 \\
 &= \sum m(0, 2, 4, 5)
 \end{aligned}$$

DeMorgan's Theorem

$$(x + y)' = x'y'$$

x	y	$\overline{x + y}$	$\bar{x} \cdot \bar{y}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

 Complement of Sum =
Product of Complement



$$(xy)' = x' + y'$$

x	y	\overline{xy}	$\bar{x} + \bar{y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

Complement of Product
= Sum of Complement



Common mistake! $(xy)' \neq x'y'$ and $(x + y)' \neq x' + y'$


Product of Sums

- Sum terms: One or more literals connected by OR operator.

$$x, x + y', y + z', x + y + z'$$

- Standard sum terms: A sum term that includes each variable of the problem, either uncomplemented or complemented.
 
$$x + y + z, x + y' + z', x' + y + z', x' + y' + z'$$



$$f_2(a, b, c) = (a + b)(a + c)(b + c)$$

- Product of Sums (POS): A group of OR gates followed by a single AND gate.

$$(w + z)(w' + y')xy \quad 4 \text{ sum terms}$$

$$(w + z)(w' + y')x \quad 3 \text{ sum terms}$$

$$(w + z)(w' + y') \quad 2 \text{ sum terms}$$

$$(w + z) \quad 1 \text{ sum term}$$

Canonical (Standard) Form in POS

Inputs			Maxterms		Output
x	y	z	<i>Term</i>	<i>Designation</i>	$f(x, y, z)$
0	0	0	$x + y + z$	M_0	1
0	0	1	$x + y + z'$	M_1	1
0	1	0	$x + y' + z$	M_2	0
0	1	1	$x + y' + z'$	M_3	1
1	0	0	$x' + y + z$	M_4	0
1	0	1	$x' + y + z'$	M_5	1
1	1	0	$x' + y' + z$	M_6	1
1	1	1	$x' + y' + z'$	M_7	0

- Maxterms: Standard sum terms. Uncomplement = 0; Complement = 1.
- Canonical Product (Product of standard sum terms): Product of sums expression with maxterms only when output is 0

$$\begin{aligned}
 f(x, y, z) &= (x + y' + z)(x' + y + z)(x' + y' + z') \\
 &= M_2 M_4 M_7 = \prod M(2, 4, 7)
 \end{aligned}$$

Summary

➤ $\overline{m_i} = M_i$ and $\overline{M_i} = m_i$

$$\overline{m_0} = (x'y'z')' = x + y + z = M_0$$

➤ If a f is in SOP form, its complement is in POS form (*vice versa*).

$$f = xyz + xy'z$$

$$f' = (x' + y' + z')(x' + y + z')$$

➤ Canonical SOP (all minterms with output 1)

$$f = xyz + xy'z = \sum m(5, 7) \quad \text{and} \quad f' = \sum m(0, 1, 2, 3, 4, 6)$$

➤ Canonical POS (all maxterm with output 0)

$$f = \prod M(0, 1, 2, 3, 4, 6) \quad \text{and} \quad f' = \prod M(5, 7)$$

Summary (Given in Test and Exam)

Commutative	$a + b = b + a$	$ab = ba$
Associative	$a + (b + c) = (a + b) + c$	$a(bc) = (ab)c$
Identity	$a + 0 = a$	$a(1) = a$
Null	$a + 1 = 1$	$a(0) = 0$
Complement	$a + a' = 1$	$a(a') = 0$
Idempotency	$a + a = a$	$a(a) = a$
Involution	$(a')' = a$	
Distributive	$a(b + c) = ab + ac$	$a + bc = (a + b)(a + c)$
Adjacency	$ab + ab' = a$	$(a + b)(a + b') = a$
Simplification	$a + a'b = a + b$	$a(a' + b) = ab$
DeMorgan	$(a + b)' = a'b'$	$(ab)' = a' + b'$
Absorption	$a + ab = a$	$a(a + b) = a$
Consensus	$ab + a'c + bc = ab + a'c$	

Exercise

1. Express the Canonical Sum and Product based on the Truth Table provided.
2. Simplify the Function in SOP form.
3. Design the logic circuit using NAND and NOT gates.

<i>Inputs</i>			<i>Output</i>
x	y	z	$f(x, y, z)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1