

# EE2000 Logic Circuit Design

---


## Recap Lecture 4 - Combinational Functional Blocks



# Exercise (Active Low)

- Design an Active Low 4-input priority encoder whereby inputs with higher subscript numbers has higher priority.
- Output IDLE is High when all inputs are high.

Input				Output		
$I_3$	$I_2$	$I_1$	$I_0$	$A_1$	$A_0$	IDLE
1	1	1	1	X	X	1
1	1	1	0	0	0	0
1	1	0	X	0	1	0
1	0	X	X	1	0	0
0	X	X	X	1	1	0

 

# Exercise (Active Low)

Input				Output		
$I_3$	$I_2$	$I_1$	$I_0$	$A_1$	$A_0$	IDLE
1	1	1	1	X	X	1
1	1	1	0	0	0	0
1	1	0	X	0	1	0
1	0	X	X	1	0	0
0	X	X	X	1	1	0

$$\text{IDLE} = I_3 I_2 I_1 I_0$$

$$A_0 = I_3' + I_3 I_2 I_1'$$

$$= I_3' + I_2 I_1'$$

$$A_1 = I_3 I_2' + I_3'$$

$$= I_2' + I_3'$$

Simplification  
 $a' + ab = a' + b$

# Exercise (Active Low)


$$\text{IDLE} = I_3 I_2 I_1 I_0$$

$$A_0 = I'_3 + I_3 I_2 I'_1$$

$$= I'_3 + I_2 I'_1$$

$$A_1 = I_3 I'_2 + I'_3$$


$$= I'_2 + I'_3$$

 

# Exercise

Realize the function  $f(w, x, y, z) = \sum m(1, 2, 5, 7, 9, 11, 13)$  using a 2-to-1 MUX

$$w = S_0$$

 

$$f(w = 0) = y'z + xz + x'yz'$$

$$f(w = 1) = y'z + x'z$$

# Exercise

Realize the function  $f(w, x, y, z) = \sum m(1, 2, 5, 7, 9, 11, 13)$  using a 8-to-1 MUX


wxyz	F	$S_2=w, S_1=x, S_0=y$
0000	0	$I_0=z$
0001	1	
0010	1	$I_1=z'$
0011	0	
0100	0	$I_2=z$
0101	1	
0110	0	$I_3=z$
0111	1	

wxyz	F	$S_2=w, S_1=x, S_0=y$
1000	0	$I_4=z$
1001	1	
1010	0	$I_5=z$
1011	1	
1100	0	$I_6=z$
1101	1	
1110	0	$I_7=0$
1111	0	

# EE2000 Logic Circuit Design

---

## Lecture 5- VHDL

 

# Question

Which of the following identifier is illegal to be used as an entity name in VHDL?

- TwO\_gaTE    Legal
- 2\_gate      Illegal – cannot start with a number
- T2-gate     Illegal – cannot have other symbol
- \_2gate      Illegal – cannot start with underscore
- AND         Illegal – Reserved word



# Exercise

```
signal C: bit_vector (0 to 3);  
signal D: bit_vector (3 downto 0);  
signal A: bit_vector (7 downto 0);
```

```
C <= "1101";  
D <= C;  
A(6 downto 3) <= D;
```

Determine the stored value in the following bit object

```
C(0) = 1  C(1) = 1  C(2) = 0  C(3) = 1  
D(3) = 1  D(2) = 1  D(1) = 0  D(0) = 1  
A(6) = 1  A(5) = 1  A(4) = 0  A(3) = 1
```

# Exercise

Transform the following logic expression to VHDL code

1)  $f = ab' + a'b$

```
f <= a AND NOT b OR NOT a AND b;  
f <= (a AND NOT b) OR (NOT a AND b);
```

2)  $f = a(b' + a')b$

```
f <= a AND (NOT b OR NOT a) AND b;
```


# Exercise

Transform the following logic expression to VHDL code

Boolean	VHDL Boolean
$Y = \overline{AB}$	<pre>Y &lt;= NOT (A AND B) ; or Y &lt;= A NAND B ;</pre>
$Y = \overline{A + B}$	<pre>Y &lt;= NOT (A OR B) ; or Y &lt;= A NOR B ;</pre>
$Y = A + BC$	<pre>Y &lt;= A OR (B AND C) ;</pre>
$Y = C\overline{X + D}$	<pre>Y &lt;= C AND NOT (X OR D) ;</pre>
$Y = A\overline{B}C + \overline{A}\overline{B}C + \overline{A}BC$	<pre>Y &lt;= (A AND NOT B AND C) OR       (NOT A AND NOT B AND C) OR       (NOT (A AND B) AND C) ;</pre>
 
# Exercise

Write your own VHDL statement to describe the logic circuit



```
S1 <= x1 OR x2;  
S2 <= x3 AND x4;  
F <= S1 XOR S2;
```


OR

```
F <= (x1 OR x2) XOR (x3  
AND x4);
```

- The Left-hand style is more readable and traceable but needs to declare two more signals
- In contrast, the Right-hand style uses fewer lines of code but is a bit difficult for debugging
- They both have the same result after being synthesized
 
# Exercise

Write your own VHDL statement to describe the logic circuit



```
Sig1 <= x XOR y;  
Sig2 <= x AND y;  
Sig3 <= Sig1 AND Cin;  
s <= Cin XOR Sig1;  
Cout <= Sig3 OR Sig2;
```