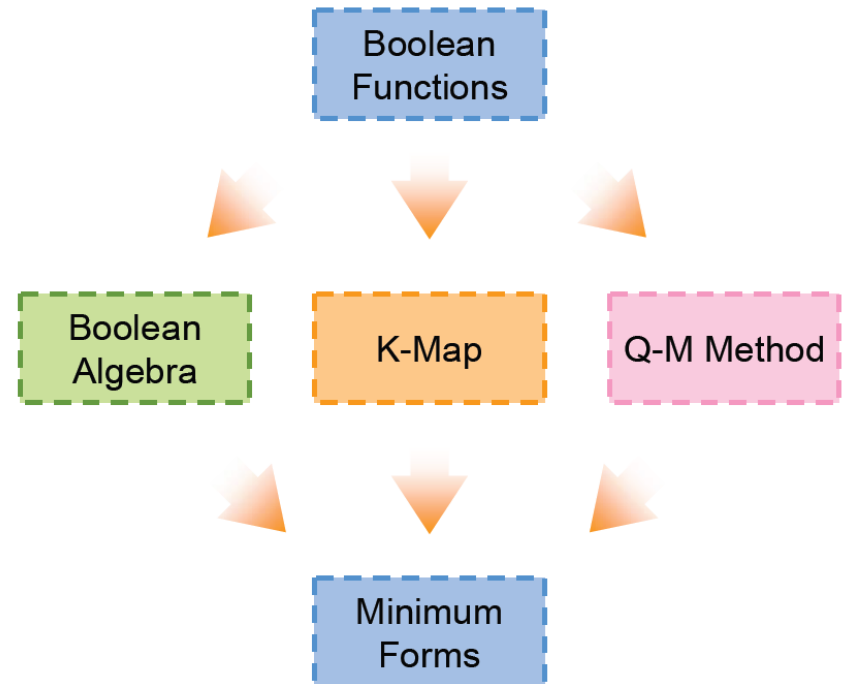



# EE2000 Logic Circuit Design

---

## Lecture 4 – Combinational Functional Blocks



# Formulation

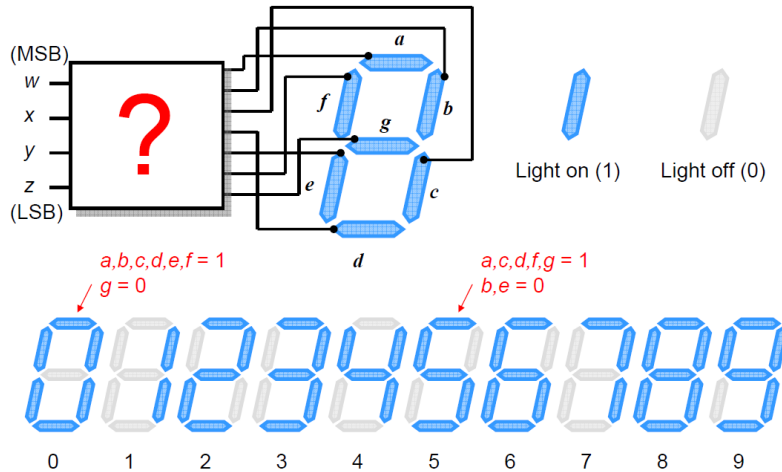

## State the case

Design a circuit to convert the BCD 8421 to the 7-segment display

- $w, x, y, z$  are the input.
- $a, b, c, d, e, f, g$  are the output.

$$a(w, x, y, z) =$$

$$\Sigma m(0, 2, 3, 5, 6, 7, 8, 9) + \Sigma d(10, 11, 12, 13, 14, 15)$$

numbers	Inputs				7-segment display						
	$w$	$x$	$y$	$z$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
10	1	0	1	0	x	x	x	x	x	x	x
11	1	0	1	1	x	x	x	x	x	x	x
12	1	1	0	0	x	x	x	x	x	x	x
13	1	1	0	1	x	x	x	x	x	x	x
14	1	1	1	0	x	x	x	x	x	x	x
15	1	1	1	1	x	x	x	x	x	x	x

# K-map for segment 'e'

$$e(w, x, y, z) = \Sigma m(0, 2, 6, 8) + \Sigma d(10, 11, 12, 13, 14, 15)$$


	<i>ab</i>	00	01	11	10
<i>cd</i>	00	$m_0$	$m_4$	$m_{12}$	$m_8$
	01	$m_1$	$m_5$	$m_{13}$	$m_9$
	11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
	10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

	<i>wx</i>	00	01	11	10
<i>yz</i>	00	1		x	1
	01			x	
	11			x	x
	10	1	1	x	x

	<i>wx</i>	00	01	11	10
<i>yz</i>	00	1		x	1
	01			x	
	11			x	x
	10	1	1	x	x


$$e(w, x, y, z) = x'z' + yz'$$

# Exercise

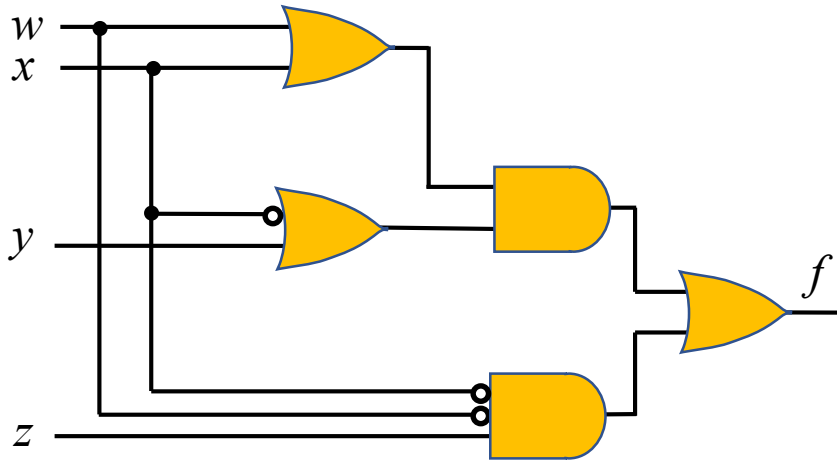

Assume that the propagation delay of NOT gate is  $\Delta\tau$  and  $2\Delta\tau$  for others .

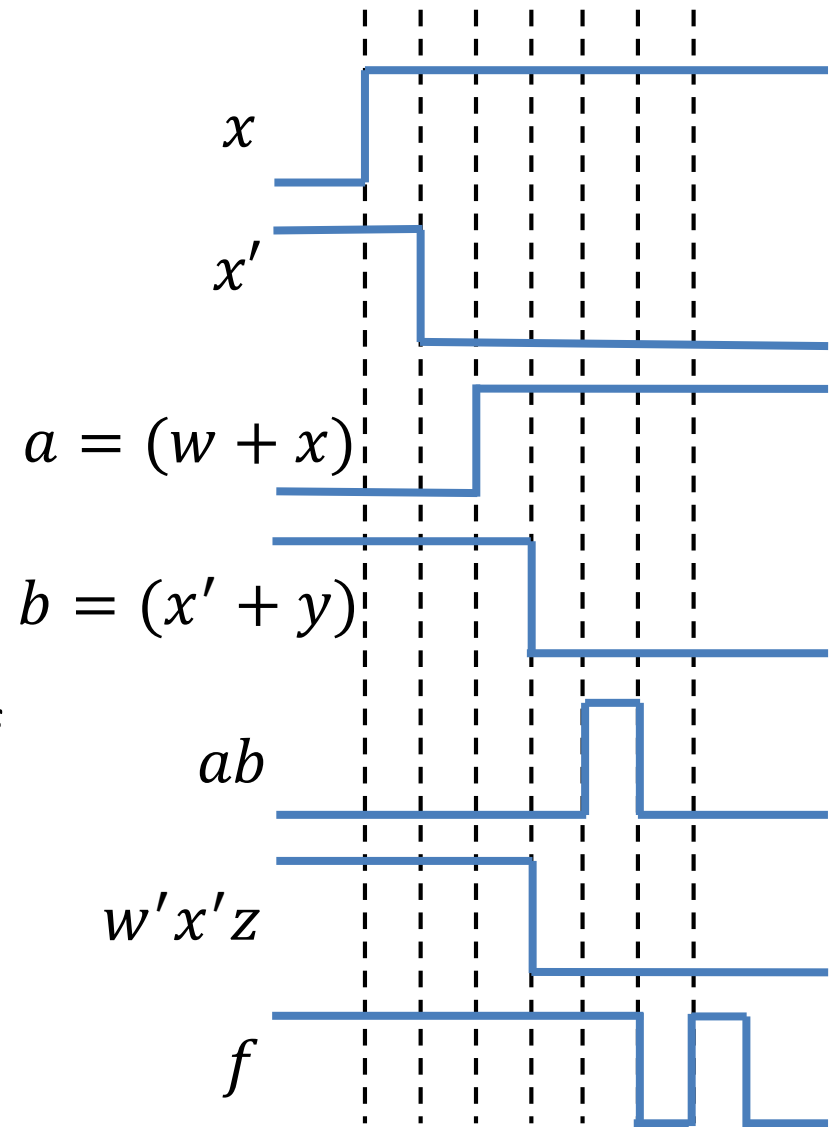Work out the timing diagram to identify the presence of any timing hazard when the input condition changes from  $(w, x, y, z) = (0,0,0,1)$  to  $(0,1,0,1)$ .



**Dynamic hazard!!!**

# Exercise

Given  $f(a, b, c) = \Sigma m(0, 2, 4, 5)$

a) Minimize the function  $f$

$c \backslash ab$		00	01	11	10
0	$m_0$	$m_2$	$m_6$	$m_4$	
1	$m_1$	$m_3$	$m_7$	$m_5$	

$c \backslash ab$		00	01	11	10
0	1	1		1	
1				1	

$ab$		00	01	11	10
$c$	0	1*	1		1
	1				1*

$$f(a, b, c) = a'c' + ab'$$

# Exercise

Given  $f(a, b, c) = \Sigma m(0, 2, 4, 5)$

b) Realize  $f$  to a hazard-free circuit

		$ab$			
		00	01	11	10
$c$	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$

		$ab$			
		00	01	11	10
$c$	0	1*	1		1
	1				1*

$$f(a, b, c) = a'c' + ab'$$

		$ab$			
		00	01	11	10
$c$	0	1	1		1
	1				1

$$f(a, b, c) = a'c' + ab' + b'c'$$

# Exercise

The following block of code is received based on an even parity, identify the errors and generate the corrected data.

1	0	1	0	0
0	0	1	1	1
1	0	0	0	1
0	0	0	1	1
1	1	0	0	0
1	0	0	0	

1	0	1	0	0
0	1	1	1	0
1	0	1	0	1
0	0	0	1	1
1	1	0	0	0
1	0	0	0	

# Exercise

1	0	1	0	0
0	0	1	1	1
1	0	0	0	1
0	0	0	1	1
1	1	0	0	0
1	0	0	0	

1	0	1	0	0
0	1	1	1	1
1	0	0	0	1
0	0	0	1	1
1	1	0	0	0
1	0	0	0	

1	0	1	0	0
0	1	1	1	0
1	0	1	0	1
0	0	0	1	1
1	1	0	0	0
1	0	0	0	

1	0	1	0	0
0	1	1	1	1
1	0	0	0	1
0	0	0	1	1
1	1	0	0	0
1	0	0	0	

or

1	0	1	0	0
0	1	0	1	0
1	0	1	0	0
0	0	0	1	1
1	1	0	0	0
1	0	0	0	



# Exercise

Determine the Hamming code using both odd and even parity bit for a data code of 11100

**Step 1:** Calculate extra bit ( $k$ ) needed for a  $n$  bit of code.

**Step 2:** Place Parity Bits in the positions of powers of 2.

Hamming Code	$H_9$	$H_8$	$H_7$	$H_6$	$H_5$	$H_4$	$H_3$	$H_2$	$H_1$
Bit									

# Exercise

Determine the Hamming code using both odd and even parity bit for a data core of 11100

For a 5-bit data  $d_5d_4d_3d_2d_1$ ,  $n = 5$

$$2^k \geq 6 + k$$

Therefore, minimum value of  $k$  is 4. We need **4 parity bits!**

# Exercise

**Step 2:** Place Parity Bits in the positions of powers of 2.

Hamming Code	$H_9$	$H_8$	$H_7$	$H_6$	$H_5$	$H_4$	$H_3$	$H_2$	$H_1$
	$d_5$	$p_4$	$d_4$	$d_3$	$d_2$	$p_3$	$d_1$	$p_2$	$p_1$
Bit	9	8	7	6	5	4	3	2	1

# Exercise

**Step 2:** Place Parity Bits in the positions of powers of 2.

Hamming Code	$H_9$	$H_8$	$H_7$	$H_6$	$H_5$	$H_4$	$H_3$	$H_2$	$H_1$
	$d_5$	$p_4$	$d_4$	$d_3$	$d_2$	$p_3$	$d_1$	$p_2$	$p_1$
Bit	9	8	7	6	5	4	3	2	1
Binary Code	1001	1000	0111	0110	0101	0100	0011	0010	0001
$p_1$									
$p_2$									
$p_3$									
$p_4$									
Even Parity									
Odd Parity									

**Step 3:** Calculate the number of '1' in each parity bits

**Step 4:** Place '1' if odd number of '1' for even parity; else '0'; Place '0' if odd number of '1' for odd parity; else '1'

# Exercise

**Step 2:** Place Parity Bits in the positions of powers of 2.

Hamming Code	$H_9$	$H_8$	$H_7$	$H_6$	$H_5$	$H_4$	$H_3$	$H_2$	$H_1$
	$d_5$	$p_4$	$d_4$	$d_3$	$d_2$	$p_3$	$d_1$	$p_2$	$p_1$
Bit	9	8	7	6	5	4	3	2	1
Binary Code	1001	1000	0111	0110	0101	0100	0011	0010	0001
$p_1$	1		1		0		0		
$p_2$			1	1			0		
$p_3$			1	1	0				
$p_4$	1								
Even Parity	1	1	1	1	0	0	0	0	0
Odd Parity	1	0	1	1	0	1	0	1	1

**Step 3:** Calculate the number of '1' in each parity bits

**Step 4:** Place '1' if odd number of '1' for even parity; else '0'; Place '0' if odd number of '1' for odd parity; else '1'

# Exercise

Example: data  $d_4d_3d_2d_1 = 1000$

Hamming Code	$H_7$	$H_6$	$H_5$	$H_4$	$H_3$	$H_2$	$H_1$
	$d_4$	$d_3$	$d_2$	$p_3$	$d_1$	$p_2$	$p_1$
Bit	7	6	5	4	3	2	1
Binary Code	0111	0110	0101	0100	0011	0010	0001
$p_1$	1		0		0		
$p_2$	1	0			0		
$p_3$	1	0	0				
Even Parity	1	0	0	1	0	1	1
Odd Parity	1	0	0	0	0	0	0

Consider odd parity and if we receive a code of 100**1**000, check the parity bits

$$c_1 = (H_7 \oplus H_5 \oplus H_3 \oplus H_1)' = (1 \oplus 0 \oplus 0 \oplus 0)' = 0$$

$$c_2 = (H_7 \oplus H_6 \oplus H_3 \oplus H_2)' = (1 \oplus 0 \oplus 0 \oplus 0)' = 0$$

$$c_3 = (H_7 \oplus H_6 \oplus H_5 \oplus H_4)' = (1 \oplus 0 \oplus 0 \oplus 1)' = 1$$

$$c_3c_2c_1 = (100)_2 = 4$$

# Exercise

$\begin{array}{r} 0 \ x \\ 0 \ y \\ (+) \ 0 \ c_{in} \\ \hline 0 \ 0 \\ c_o \ s \end{array}$	$\begin{array}{r} 0 \ x \\ 1 \ y \\ (+) \ 0 \ c_{in} \\ \hline 0 \ 1 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 0 \ y \\ (+) \ 0 \ c_{in} \\ \hline 0 \ 1 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 1 \ y \\ (+) \ 0 \ c_{in} \\ \hline 1 \ 0 \\ c_o \ s \end{array}$
$\begin{array}{r} 0 \ x \\ 0 \ y \\ (+) \ 1 \ c_{in} \\ \hline 0 \ 1 \\ c_o \ s \end{array}$	$\begin{array}{r} 0 \ x \\ 1 \ y \\ (+) \ 1 \ c_{in} \\ \hline 1 \ 0 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 0 \ y \\ (+) \ 1 \ c_{in} \\ \hline 1 \ 0 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 1 \ y \\ (+) \ 1 \ c_{in} \\ \hline 1 \ 1 \\ c_o \ s \end{array}$

Inputs			Outputs	
$x$	$y$	$c_{in}$	$c_o$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Work out the algebraic functions of  $s$  and  $c_o$  using K-map
- Draw the logic circuit diagram of full adder

	$ab$	00	01	11	10
$c$					
0		$m_0$	$m_2$	$m_6$	$m_4$
1		$m_1$	$m_3$	$m_7$	$m_5$

# Exercise

		$xy$			
$c_o$	$c_{in}$	00	01	11	10
	0			1	
	1		1	1	1

$$\begin{aligned}
 c_o &= xy + xc_{in} + yc_{in} = xy + c_{in}(x + y) \\
 &= xy + c_{in}(xy' + x'y + xy) \\
 &= xy(1 + c_{in}) + c_{in}(xy' + x'y) \\
 &= xy + c_{in}(x \oplus y)
 \end{aligned}$$

		$xy$			
$s$	$c_{in}$	00	01	11	10
	0		1		1
	1	1		1	


$$\begin{aligned}
 s &= x'y'c_{in} + xyc_{in} + x'y'c'_{in} + xy'c'_{in} \\
 &= c_{in}(x'y' + xy) + c'_{in}(x'y + xy') \\
 &= c_{in}(x \oplus y)' + c'_{in}(x \oplus y) \\
 &= c_{in} \oplus (x \oplus y)
 \end{aligned}$$



# Exercise

c \ ab	00	01	11	10
	0	1	1	0
0	$m_0$	$m_2$	$m_6$	$m_4$
1	$m_1$	$m_3$	$m_7$	$m_5$
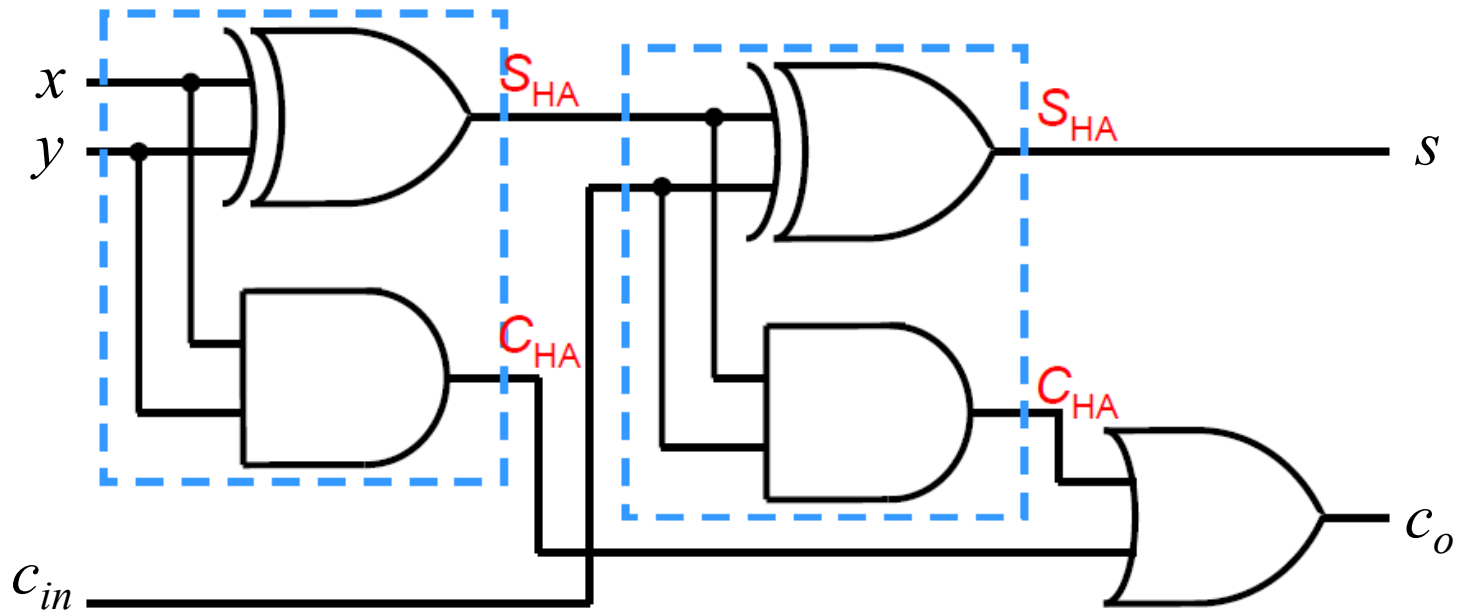
$$c_o = xy + c_{in}(x \oplus y) \quad s = c_{in} \oplus (x \oplus y)$$



# Exercise

$b_o$	0	0	$x$
(-)		0	$y$
(-)		0	$b_{in}$
<hr/>			
	0		
	$d$		

$b_o$	1	0	$x$
(-)		1	$y$
(-)		0	$b_{in}$
<hr/>			
	1		
	$d$		

$b_o$	0	1	$x$
(-)		0	$y$
(-)		0	$b_{in}$
<hr/>			
	1		
	$d$		

$b_o$	0	1	$x$
(-)		1	$y$
(-)		0	$b_{in}$
<hr/>			
	0		
	$d$		

$b_o$	1	0	$x$
(-)		0	$y$
(-)		1	$b_{in}$
<hr/>			
	1		
	$d$		

$b_o$	1	0	$x$
(-)		1	$y$
(-)		1	$b_{in}$
<hr/>			
	0		
	$d$		

$b_o$	0	1	$x$
(-)		0	$y$
(-)		1	$b_{in}$
<hr/>			
	0		
	$d$		

$b_o$	1	1	$x$
(-)		1	$y$
(-)		1	$b_{in}$
<hr/>			
	1		
	$d$		

Inputs			Outputs	
$x$	$y$	$b_{in}$	$b_o$	$d$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

- Work out the algebraic functions of  $d$  and  $b_o$  using K-map
- Draw the logic circuit diagram of full subtractor

	$a$	$b$	00	01	11	10
$c$	0		$m_0$	$m_2$	$m_6$	$m_4$
	1		$m_1$	$m_3$	$m_7$	$m_5$

# Exercise

c \ ab	00	01	11	10
0	$m_0$	$m_2$	$m_6$	$m_4$
1	$m_1$	$m_3$	$m_7$	$m_5$

$b_o$ \ $b_{in} \ xy$	00	01	11	10
0		1		
1	1	1	1	

$$\begin{aligned}
 b_o &= x'y + x'b_{in} + yb_{in} = x'y + b_{in}(x' + y) \\
 &= x'y + b_{in}(x'y' + x'y + xy) \\
 &= x'y(1 + b_{in}) + b_{in}(x'y' + xy) \\
 &= x'y + b_{in}(x \oplus y)'
 \end{aligned}$$


$d$ \ $b_{in} \ xy$	00	01	11	10
0		1		1
1	1		1	

$$\begin{aligned}
 d &= x'y'b_{in} + xyb_{in} + x'yb'_{in} + xy'b'_{in} \\
 &= b_{in}(x'y' + xy) + b'_{in}(x'y + xy') \\
 &= b_{in}(x \oplus y)' + b'_{in}(x \oplus y) \\
 &= b_{in} \oplus (x \oplus y)
 \end{aligned}$$


# Exercise

		<i>ab</i>			
		00	01	11	10
<i>c</i>	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$
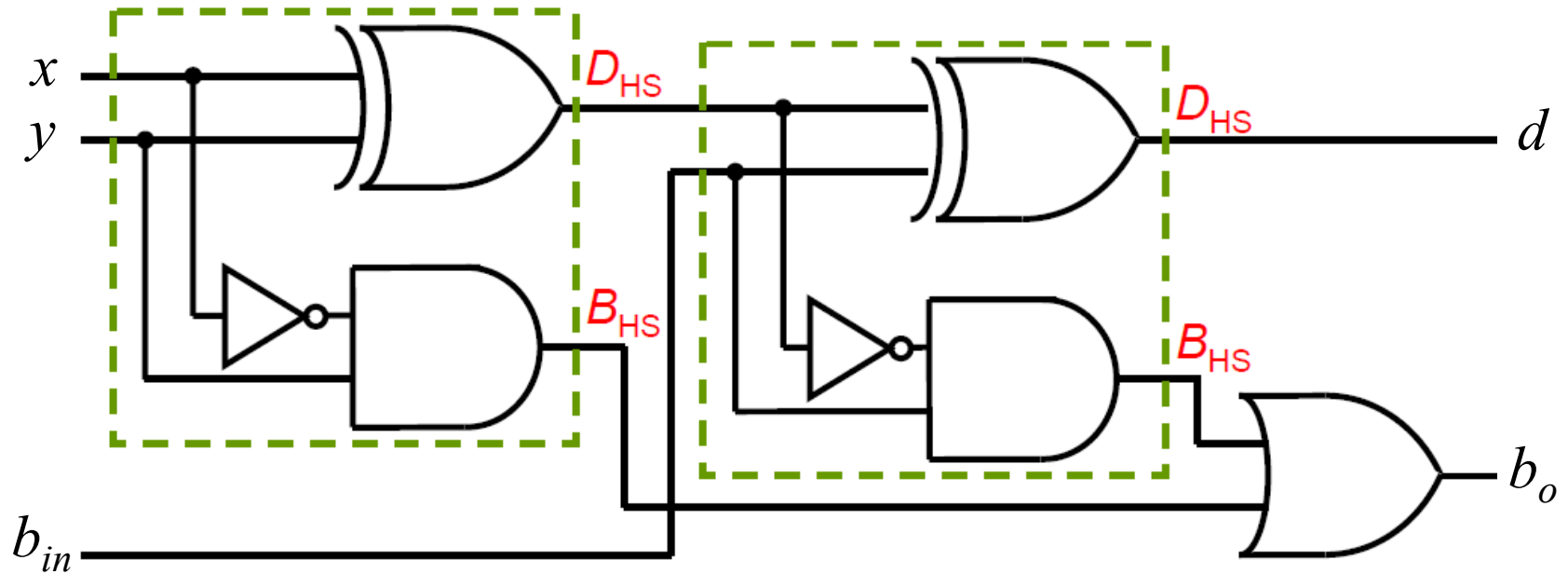
$$b_o = x'y + b_{in}(x \oplus y)' \quad d = b_{in} \oplus (x \oplus y)$$



# Exercise (Decimal-to-Binary Encoder)

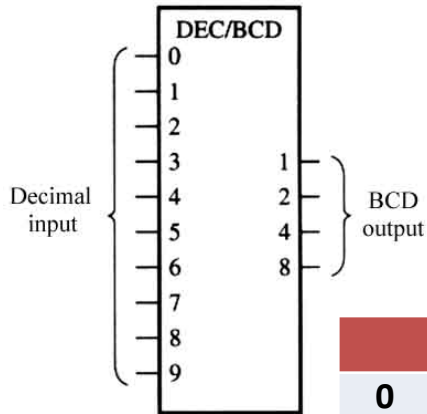

Inputs										Outputs			
0	1	2	3	4	5	6	7	8	9	$A_3$	$A_2$	$A_1$	$A_0$
1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	0	0	1	0	0
0	0	0	0	0	1	0	0	0	0	0	1	0	1
0	0	0	0	0	0	1	0	0	0	0	1	1	0
0	0	0	0	0	0	0	1	0	0	0	1	1	1
0	0	0	0	0	0	0	0	1	0	1	0	0	0
0	0	0	0	0	0	0	0	0	1	1	0	0	1

# Exercise (Decimal-to-Binary Encoder)

Inputs										Outputs			
0	1	2	3	4	5	6	7	8	9	$A_3$	$A_2$	$A_1$	$A_0$
1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	0	0	1	0	0
0	0	0	0	0	1	0	0	0	0	0	1	0	1
0	0	0	0	0	0	1	0	0	0	0	1	1	0
0	0	0	0	0	0	0	1	0	0	0	1	1	1
0	0	0	0	0	0	0	0	1	0	1	0	0	0
0	0	0	0	0	0	0	0	0	1	1	0	0	1

