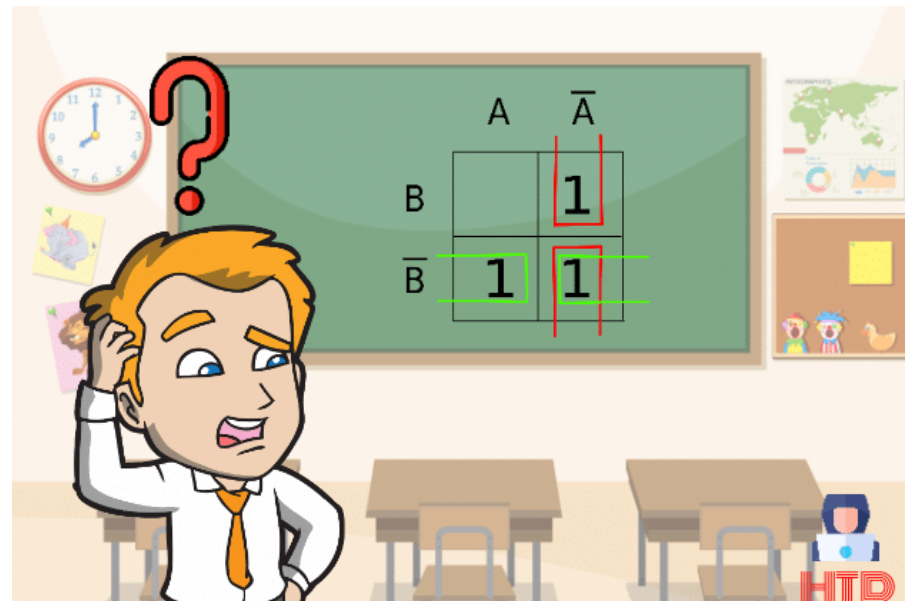


EE2000 Logic Circuit Design



Recap Lecture 2 – Karnaugh Map and Quine-McCluskey (QM) Method



2.1 Karnaugh Map


- In 1953, Maurice Karnaugh introduced a map method known as **Karnaugh map (K-map)**
- A straightforward procedure for minimizing Boolean functions in a tabular form
- **Graphical** representation of a truth table
- **Minterm** is used in the cell of the K-map
- n -variable function has 2^n cells:
 - Two-variable K-map has 4 cells
 - Three-variable K-map has 8 cells
 - Four-variable K-map has 16 cells

Four-variable K-map

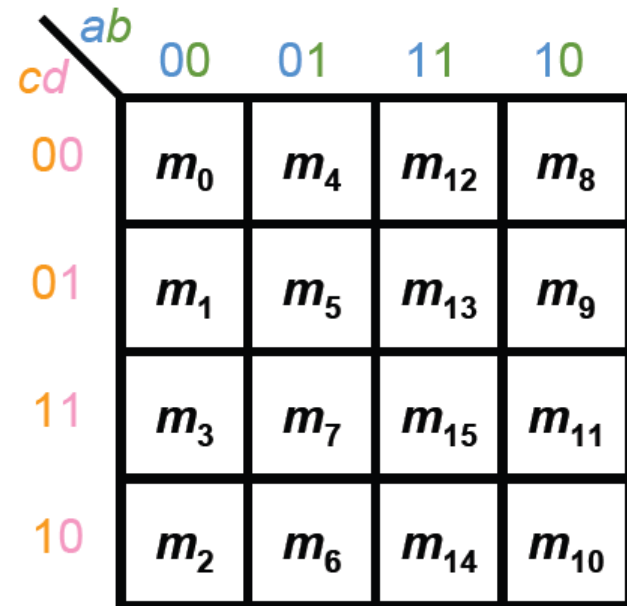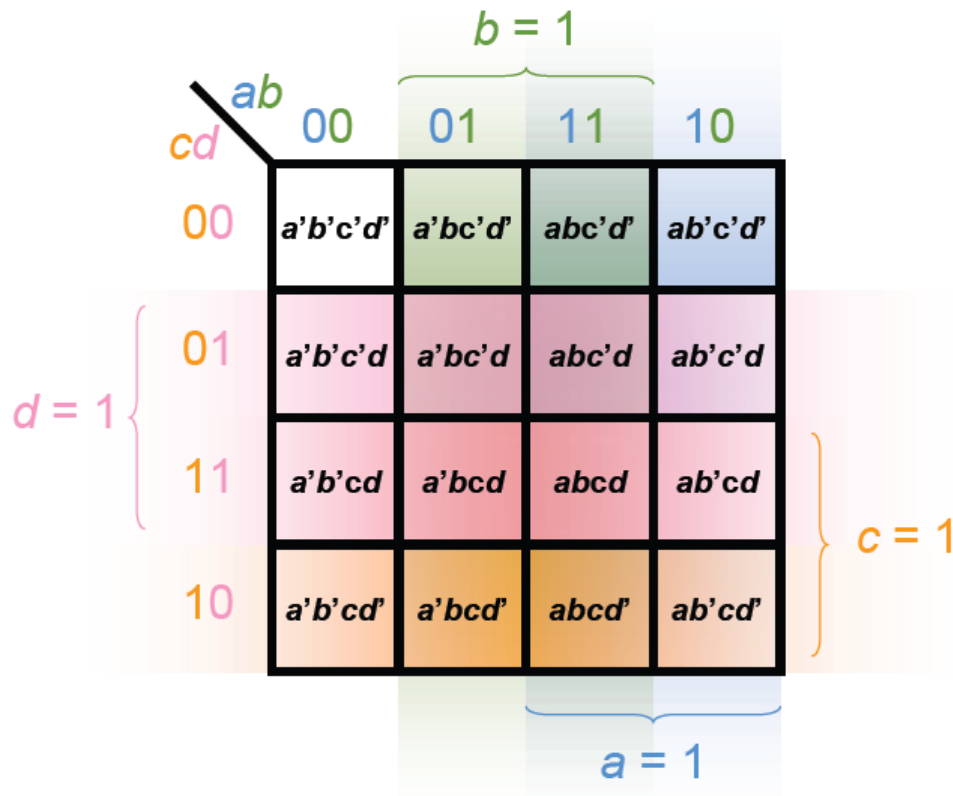


Note the Gray code order of the rows and columns

Summary

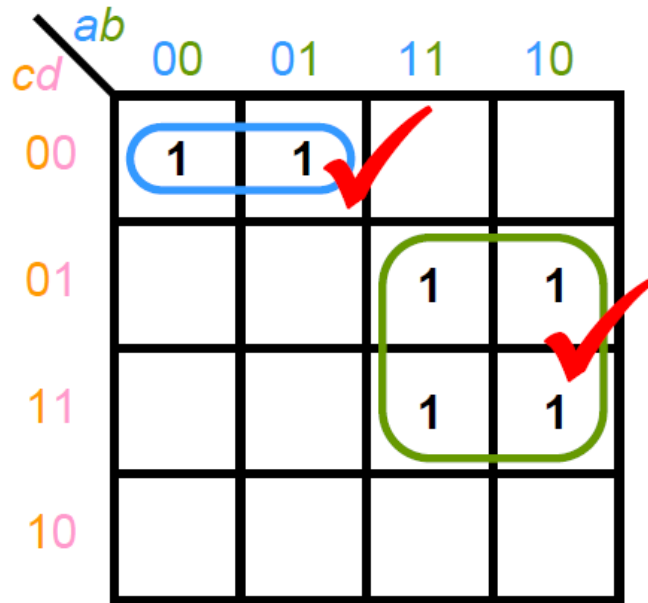

Group size is power of 2 (e.g. 2, 4, 8)

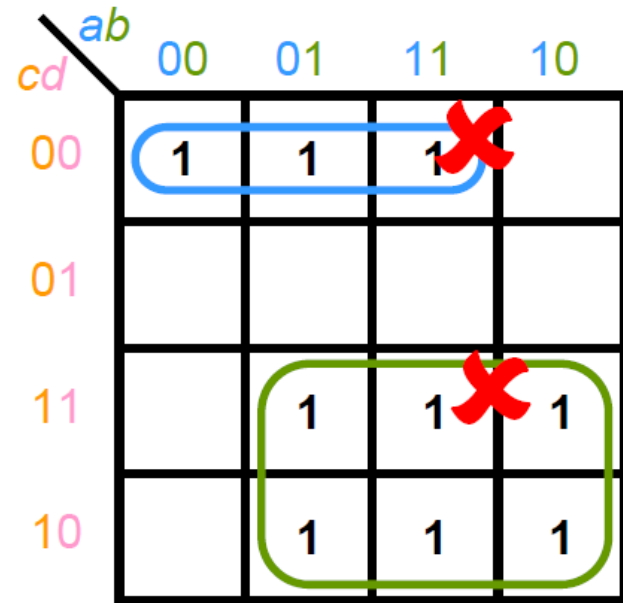

Other group size is illegal


- Booleans function to be minimized by K-map are always in Canonical SOP or POS (will discuss later) form
- Arrange cells in 1-bit difference
- Group adjacent cells in group size of 2^n , e.g. 2, 4, 8
- Apply adjacency law

2.2 Minimization using Karnaugh Map

- Group adjacent cells in group size of 2^n , e.g. 2, 4, 8
- Rules:
 1. Find the fewest groups that can cover all cells marked with 1s.
 2. The groups should be as large as possible.
- Goal:
 1. Reduce the number of product terms to minimum
 2. Save the cost


Terminology

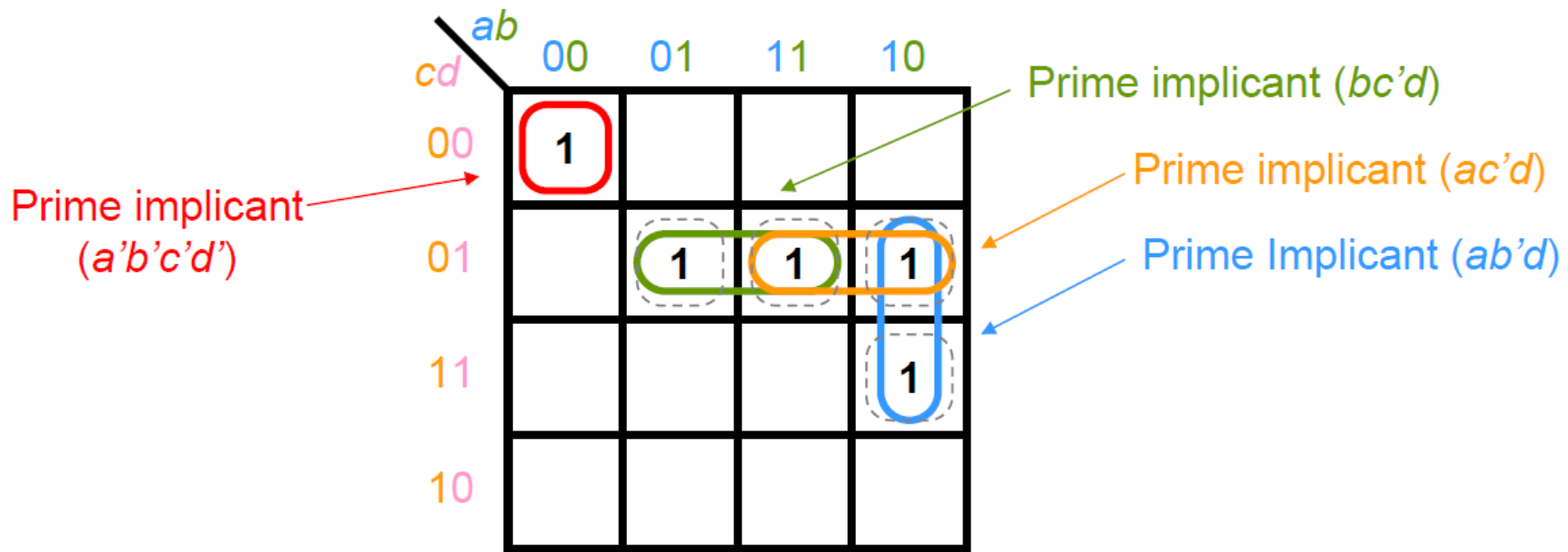Prime Implicant: An implicant that is not fully contained in any one other implicant.



Terminology

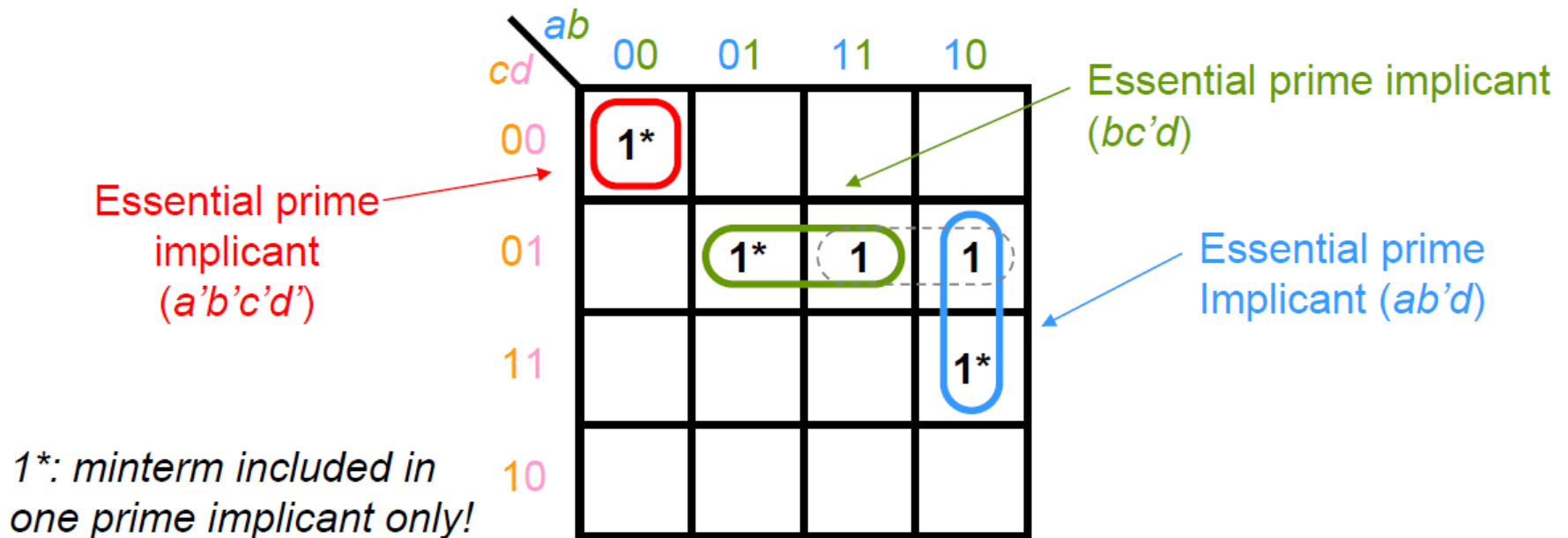Essential Prime Implicant: If a minterm is included in only one prime implicant, that prime implicant is essential prime implicant.



Systematic Approach

➤ Rules:



1. Find the fewest groups that can cover all cells marked with 1s.
2. The groups should be as large as possible.

➤ Approach:

1. Determine all PIs.
2. Select EPIs.
3. Add PI to include the remaining minterm.

Exercise

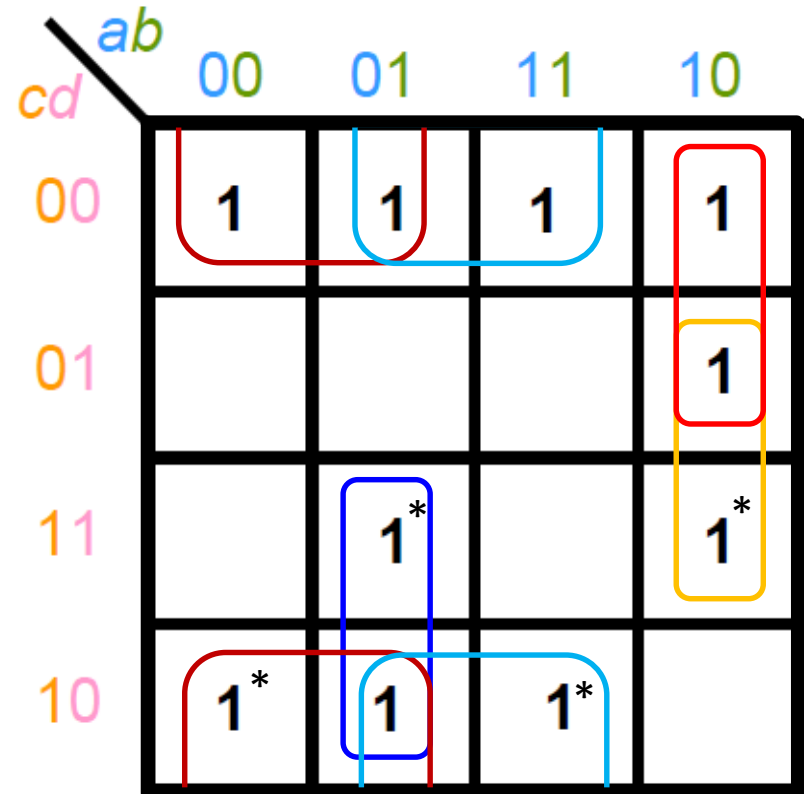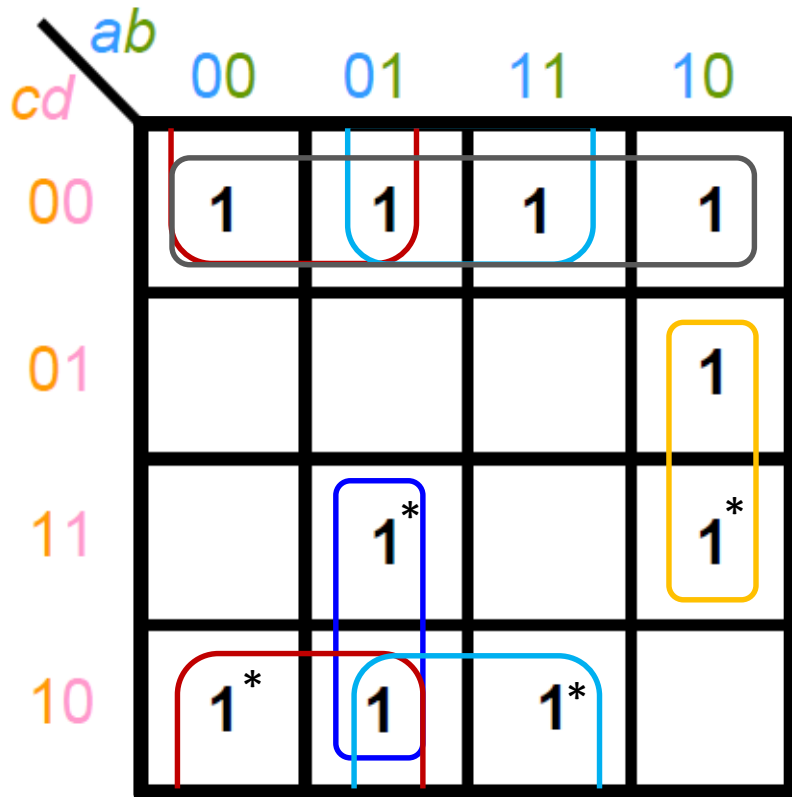1. Identify all PIs.
2. Select all EPIs.
3. Add PIs of remaining minterms.



POS

Simplify $f(a, b, c, d) = \Sigma m(0, 1, 2, 5, 8, 9, 10)$ in POS form

| | | | | |
|------|------|----|----|----|
| | ab | | | |
| | 00 | 01 | 11 | 10 |
| cd | | | | |
| 00 | 1 | 0 | 0 | 1 |
| 01 | 1 | 1 | 0 | 1 |
| 11 | 0 | 0 | 0 | 0 |
| 10 | 1 | 0 | 0 | 1 |

Fill the 1s and 0s into the map

| | | | | |
|------|------|----|----|----|
| | ab | | | |
| | 00 | 01 | 11 | 10 |
| cd | | | | |
| 00 | 1 | 0 | 0 | 1 |
| 01 | 1 | 1 | 0 | 1 |
| 11 | 0 | 0 | 0 | 0 |
| 10 | 1 | 0 | 0 | 1 |

Group the 0s using the same procedure as grouping the 1s

$$f'(a, b, c, d) = ab + cd + bd'$$

$$f(a, b, c, d) = (a'+b')(c'+d')(b'+d)$$

2.3 Boolean Functions with Don't Care Cases

The output of Boolean functions are **incompletely specified functions**,

- For some input conditions, the outputs are unspecified
- Input condition has no effects to the function
- Output values are defined as **don't Care**
- Don't Care term can be minterm / maxterms
- Don't Care term indicates by an x , d , ϕ or φ

Solutions

1. Identify PIs that must include all 1s but don't care term \times is optional.
2. Use \times when possible to create larger group size.
3. Select the EPIs first, then remaining PIs

| | | | | |
|---------|------------------------------|---|---|---|
| | ab 00 01 11 10 | | | |
| cd 00 | X | 0 | 0 | 0 |
| 01 | 1 | X | 0 | 0 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | X | 0 | 0 | 0 |

$$f(a, b, c, d) = a'b' + cd$$

| | | | | |
|---------|------------------------------|---|---|---|
| | ab 00 01 11 10 | | | |
| cd 00 | X | 0 | 0 | 0 |
| 01 | 1 | X | 0 | 0 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | X | 0 | 0 | 0 |

$$f(a, b, c, d) = a'd + cd$$

Choose to include those Xs that give largest PIs

2.4 Quine-McCluskey (QM) Method

- Developed by W. V. Quine and E. J. McCluskey in 1956
- Functionally identical to Karnaugh map
- More efficient in computer algorithms
- Ease to handle large number of variables

For number of variables that is less than or equal to 4, we use K-map; otherwise, QM method will be more efficient.

Procedure of QM-method (4-variable)

Step 1: Partition (Group minterms by the number of 1's)

| w | x | y | z | Minterms |
|-----|-----|-----|-----|----------|
| 0 | 0 | 0 | 0 | m_0 |
| 0 | 0 | 0 | 1 | m_1 |
| 0 | 0 | 1 | 0 | m_2 |
| 0 | 0 | 1 | 1 | m_3 |
| 0 | 1 | 0 | 0 | m_4 |
| 0 | 1 | 0 | 1 | m_5 |
| 0 | 1 | 1 | 0 | m_6 |
| 0 | 1 | 1 | 1 | m_7 |
| 1 | 0 | 0 | 0 | m_8 |
| 1 | 0 | 0 | 1 | m_9 |
| 1 | 0 | 1 | 0 | m_{10} |
| 1 | 0 | 1 | 1 | m_{11} |
| 1 | 1 | 0 | 0 | m_{12} |
| 1 | 1 | 0 | 1 | m_{13} |
| 1 | 1 | 1 | 0 | m_{14} |
| 1 | 1 | 1 | 1 | m_{15} |



| Minterms | $wxyz$ |
|----------|--------|
| m_0 | 0000 |
| m_1 | 0001 |
| m_2 | 0010 |
| m_4 | 0100 |
| m_8 | 1000 |
| m_3 | 0011 |
| m_5 | 0101 |
| m_6 | 0110 |
| m_9 | 1001 |
| m_{10} | 1010 |
| m_{12} | 1100 |
| m_7 | 0111 |
| m_{11} | 1011 |
| m_{13} | 1101 |
| m_{14} | 1110 |
| m_{15} | 1111 |

Procedure of QM-method (4-variable)

Step 1: Partition (Group minterms by the number of 1's)

Simplify $f(a, b, c, d) = \sum m(1, 4, 5, 6, 8, 9, 10, 12, 14)$

| Minterms | $abcd$ |
|----------|--------|
| m_1 | 0001 |
| m_4 | 0100 |
| m_8 | 1000 |
| m_5 | 0101 |
| m_6 | 0110 |
| m_9 | 1001 |
| m_{10} | 1010 |
| m_{12} | 1100 |
| m_{14} | 1110 |

Procedure of QM-method (4-variable)

Step 2: Combine (Apply adjacency property to each pair of terms in consecutive groups)

- Combine adjacent group implicants into $(n-1)$ variable implicants
- Mark the changed bit with “-” and tick the combined implicants

| Minterms | <i>abcd</i> |
|----------|-------------|
| m_1 | 0001 ✓ |
| m_4 | 0100 |
| m_8 | 1000 |
| m_5 | 0101 ✓ |
| m_6 | 0110 |
| m_9 | 1001 ✓ |
| m_{10} | 1010 |
| m_{12} | 1100 |
| m_{14} | 1110 |

| Minterms | <i>abcd</i> |
|------------|-------------|
| m_1, m_5 | 0-01 |
| m_1, m_9 | -001 |

Procedure of QM-method (4-variable)

Step 2: Combine (Apply adjacency property to each pair of terms in consecutive groups)

- Combine adjacent group implicants into $(n-1)$ variable implicants
- Mark the changed bit with “-” and tick the combined implicants

| Minterms | <i>abcd</i> |
|----------|-------------|
| m_1 | 0001 ✓ |
| m_4 | 0100 ✓ |
| m_8 | 1000 ✓ |
| m_5 | 0101 ✓ |
| m_6 | 0110 ✓ |
| m_9 | 1001 ✓ |
| m_{10} | 1010 ✓ |
| m_{12} | 1100 ✓ |
| m_{14} | 1110 ✓ |

| Minterms | <i>abcd</i> |
|------------------|-------------|
| m_1, m_5 | 0-01 |
| m_1, m_9 | -001 |
| m_4, m_5 | 010- |
| m_4, m_6 | 01-0 ✓ |
| m_4, m_{12} | -100 ✓ |
| m_8, m_9 | 100- |
| m_8, m_{10} | 10-0 |
| m_8, m_{12} | 1-00 |
| m_6, m_{14} | -110 ✓ |
| m_{10}, m_{14} | 1-10 |
| m_{12}, m_{14} | 11-0 ✓ |

| Minterms | <i>abcd</i> |
|----------------------------|-------------|
| m_4, m_6, m_{12}, m_{14} | -1-0 |

Procedure of QM-method (4-variable)

Step 3: Identify Prime Implicants (PIs)

-All unmarked terms

| Minterms | <i>abcd</i> |
|----------|-------------|
| m_1 | 0001 ✓ |
| m_4 | 0100 ✓ |
| m_8 | 1000 ✓ |
| m_5 | 0101 ✓ |
| m_6 | 0110 ✓ |
| m_9 | 1001 ✓ |
| m_{10} | 1010 ✓ |
| m_{12} | 1100 ✓ |
| m_{14} | 1110 ✓ |

| Minterms | <i>abcd</i> |
|------------------|-------------|
| m_1, m_5 | 0-01 PI_3 |
| m_1, m_9 | -001 PI_4 |
| m_4, m_5 | 010- PI_5 |
| m_4, m_6 | 01-0 ✓ |
| m_4, m_{12} | -100 ✓ |
| m_8, m_9 | 100- PI_6 |
| m_8, m_{10} | 10-0 ✓ |
| m_8, m_{12} | 1-00 ✓ |
| m_6, m_{14} | -110 ✓ |
| m_{10}, m_{14} | 1-10 ✓ |
| m_{12}, m_{14} | 11-0 ✓ |

| Minterms | <i>abcd</i> |
|-------------------------------|-------------|
| m_4, m_6, m_{12}, m_{14} | -1-0 PI_1 |
| $m_8, m_{10}, m_{12}, m_{14}$ | 1--0 PI_2 |

Procedure of QM-method (4-variable)

Step 4: Generate PI chart

- Identify minterms that are covered by only 1 PI
- Identify essential PIs

$$f(a, b, c, d) = \Sigma m(1, 4, 5, 6, 8, 9, 10, 12, 14)$$

| PI | Minterms | <i>abcd</i> | 1 | 4 | 5 | 6 | 8 | 9 | 10 | 12 | 14 |
|-----------------|-------------------------------|-------------|---|---|---|---|---|---|----|----|----|
| PI ₁ | m_4, m_6, m_{12}, m_{14} | -1-0 | | x | | x | | | | x | x |
| PI ₂ | $m_8, m_{10}, m_{12}, m_{14}$ | 1--0 | | | | | x | | x | x | x |
| PI ₃ | m_1, m_5 | 0-01 | x | | x | | | | | | |
| PI ₄ | m_1, m_9 | -001 | x | | | | | x | | | |
| PI ₅ | m_4, m_5 | 010- | | x | x | | | | | | |
| PI ₆ | m_8, m_9 | 100- | | | | | x | x | | | |

Procedure of QM-method (4-variable)

Step 4: Generate PI chart

- Identify minterms that are covered by only 1 PI
- Identify essential PIs

| PI | Minterms | $abcd$ | 1 | 4 | 5 | 6 | 8 | 9 | 10 | 12 | 14 |
|--------|-------------------------------|--------|---|---|---|---|---|---|----|----|----|
| PI_1 | m_4, m_6, m_{12}, m_{14} | -1-0 | | x | | x | | | | x | x |
| PI_2 | $m_8, m_{10}, m_{12}, m_{14}$ | 1--0 | | | | | x | | x | x | x |
| PI_3 | m_1, m_5 | 0-01 | x | | x | | | | | | |
| PI_4 | m_1, m_9 | -001 | x | | | | | x | | | |
| PI_5 | m_4, m_5 | 010- | | x | x | | | | | | |
| PI_6 | m_8, m_9 | 100- | | | | | x | x | | | |

$\therefore PI_1$ and PI_2 are essential PIs.

Procedure of QM-method (4-variable)

Step 5: Reduce PI chart

- Remove the rows of EPIs and the columns that covered by them

| PI | Minterms | <i>abcd</i> | 1 | 5 | 9 |
|-----------------|------------|-------------|---|---|---|
| PI ₃ | m_1, m_5 | 0-01 | x | x | |
| PI ₄ | m_1, m_9 | -001 | x | | x |
| PI ₅ | m_4, m_5 | 010- | | x | |
| PI ₆ | m_8, m_9 | 100- | | | x |

Solution 1

| PI | Minterms | <i>abcd</i> | 1 | 5 | 9 |
|-----------------|------------|-------------|---|---|---|
| PI ₃ | m_1, m_5 | 0-01 | x | x | |
| PI ₄ | m_1, m_9 | -001 | x | | x |

Solution 2

| PI | Minterms | <i>abcd</i> | 1 | 5 | 9 |
|-----------------|------------|-------------|---|---|---|
| PI ₃ | m_1, m_5 | 0-01 | x | x | |
| PI ₆ | m_8, m_9 | 100- | | | x |

Solution 3

| PI | Minterms | <i>abcd</i> | 1 | 5 | 9 |
|-----------------|------------|-------------|---|---|---|
| PI ₄ | m_1, m_9 | -001 | x | | x |
| PI ₅ | m_4, m_5 | 010- | | x | |

Procedure of QM-method (4-variable)

Step 6: Express the Boolean Function

| PI | Minterms | $abcd$ |
|--------|-------------------------------|--------|
| PI_1 | m_4, m_6, m_{12}, m_{14} | -1-0 |
| PI_2 | $m_8, m_{10}, m_{12}, m_{14}$ | 1--0 |
| PI_3 | m_1, m_5 | 0-01 |
| PI_4 | m_1, m_9 | -001 |

$$\begin{aligned}f(a, b, c, d) &= PI_1 + PI_2 + PI_3 + PI_4 \\&= bd' + ad' + a'c'd + b'c'd\end{aligned}$$

| PI | Minterms | $abcd$ |
|--------|-------------------------------|--------|
| PI_1 | m_4, m_6, m_{12}, m_{14} | -1-0 |
| PI_2 | $m_8, m_{10}, m_{12}, m_{14}$ | 1--0 |
| PI_3 | m_1, m_5 | 0-01 |
| PI_6 | m_8, m_9 | 100- |

$$\begin{aligned}f(a, b, c, d) &= PI_1 + PI_2 + PI_3 + PI_6 \\&= bd' + ad' + a'c'd + ab'c'\end{aligned}$$

| PI | Minterms | $abcd$ |
|--------|-------------------------------|--------|
| PI_1 | m_4, m_6, m_{12}, m_{14} | -1-0 |
| PI_2 | $m_8, m_{10}, m_{12}, m_{14}$ | 1--0 |
| PI_4 | m_1, m_9 | -001 |
| PI_5 | m_4, m_5 | 010- |

$$\begin{aligned}f(a, b, c, d) &= PI_1 + PI_2 + PI_4 + PI_5 \\&= bd' + ad' + b'c'd + a'bc'\end{aligned}$$

Exercise (Don't Care Case)

Step 1-3 (Partition, Combine, List Pls): Include Don't Care minterms

Simplify $f(a, b, c, d) = \Sigma m(4, 8, 9, 10, 12, 15) + \Sigma d(2, 6, 13)$

| Minterms | $abcd$ |
|----------|--------|
| m_2 | 0010 ✓ |
| m_4 | 0100 ✓ |
| m_8 | 1000 ✓ |
| m_6 | 0110 ✓ |
| m_9 | 1001 ✓ |
| m_{10} | 1010 ✓ |
| m_{12} | 1100 ✓ |
| m_{13} | 1101 ✓ |
| m_{15} | 1111 ✓ |

| Minterms | $abcd$ |
|------------------|-------------|
| m_2, m_6 | 0-10 PI_2 |
| m_2, m_{10} | -010 PI_3 |
| m_4, m_6 | 01-0 PI_4 |
| m_4, m_{12} | -100 PI_5 |
| m_8, m_9 | 100- ✓ |
| m_8, m_{10} | 10-0 PI_6 |
| m_8, m_{12} | 1-00 ✓ |
| m_9, m_{13} | 1-01 ✓ |
| m_{12}, m_{13} | 110- ✓ |
| m_{13}, m_{15} | 11-1 PI_7 |

| Minterms | $abcd$ |
|----------------------------|-------------|
| m_8, m_9, m_{12}, m_{13} | 1-0- PI_1 |

Exercise (Don't Care Case)


Step 4: Generate PI chart

- Exclude Don't Care Minterms

Simplify $f(a, b, c, d) = \Sigma m(4, 8, 9, 10, 12, 15) + \Sigma d(2, 6, 13)$

| PI | Minterms | <i>abcd</i> | 4 | 8 | 9 | 10 | 12 | 15 |
|-----------------|----------------------------|-------------|---|---|---|----|----|----|
| PI ₁ | m_8, m_9, m_{12}, m_{13} | 1-0- | | | | | | |
| PI ₂ | m_2, m_6 | 0-10 | | | | | | |
| PI ₃ | m_2, m_{10} | -010 | | | | | | |
| PI ₄ | m_4, m_6 | 01-0 | | | | | | |
| PI ₅ | m_4, m_{12} | -100 | | | | | | |
| PI ₆ | m_8, m_{10} | 10-0 | | | | | | |
| PI ₇ | m_{13}, m_{15} | 11-1 | | | | | | |

Summary

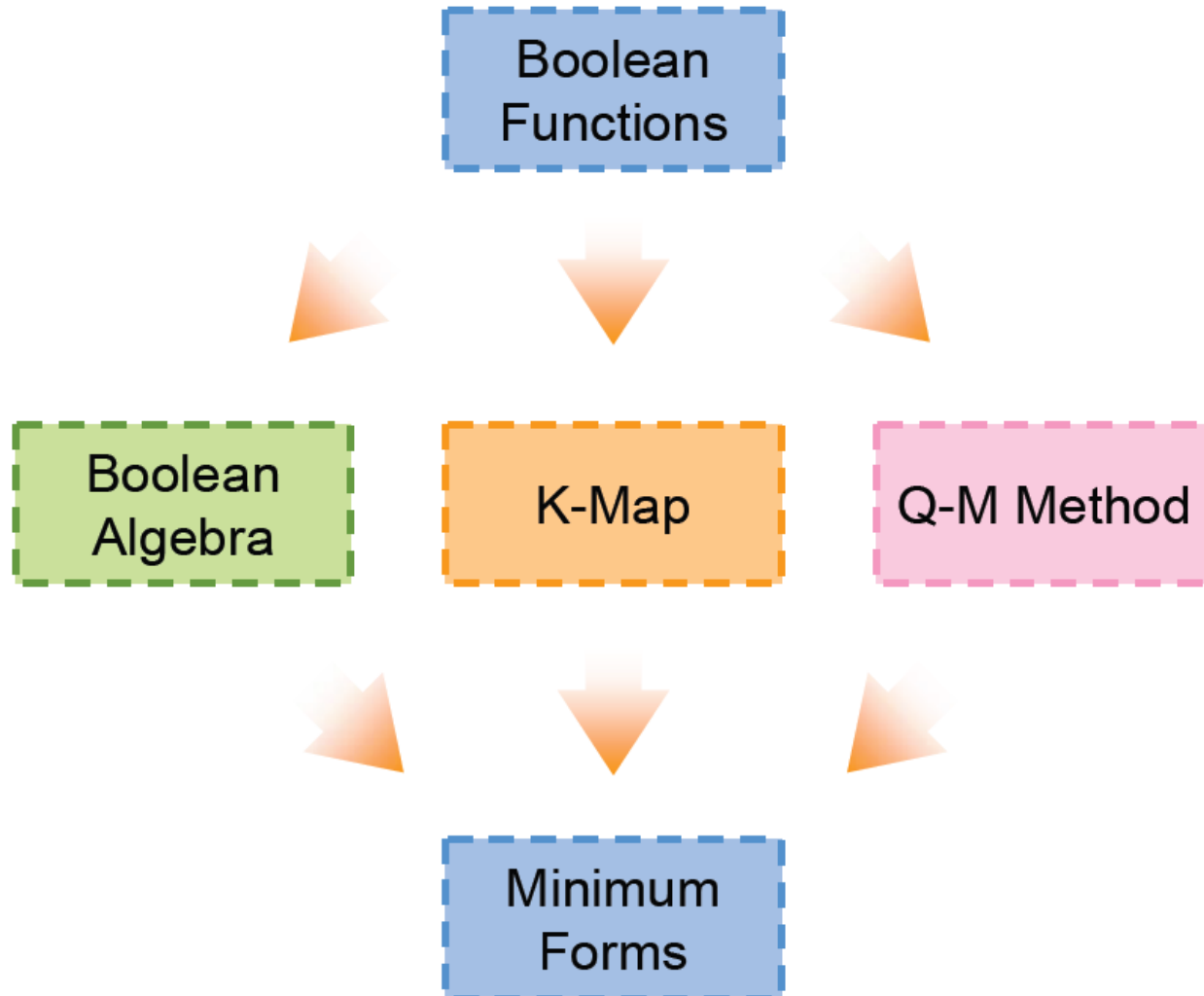

Multiple Output Problems

| c \ ab | 00 | 01 | 11 | 10 |
|--------|-------|-------|-------|-------|
| | m_0 | m_2 | m_6 | m_4 |
| 0 | | | | |
| 1 | | | | |

$$f(a, b, c) = \sum m(2, 3, 7)$$

| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| | | | | |
| 0 | | 1 | | |
| 1 | | 1 | 1 | |

$$g(a, b, c) = \sum m(4, 5, 7)$$

| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| | | | | |
| 0 | | | | 1 |
| 1 | | | 1 | 1 |

Multiple Output Problems

$$f(a, b, c) = \sum m(2, 3, 7)$$

| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| | | | | |
| 0 | | 1 | | |
| 1 | | 1 | 1 | |

$$f(a, b, c) = a'b + bc$$


$$g(a, b, c) = \sum m(4, 5, 7)$$

| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| | | | | |
| 0 | | | | 1 |
| 1 | | | 1 | 1 |


$$g(a, b, c) = ab' + ac$$

Multiple Output Problems

$$f(a, b, c) = a'b + bc$$

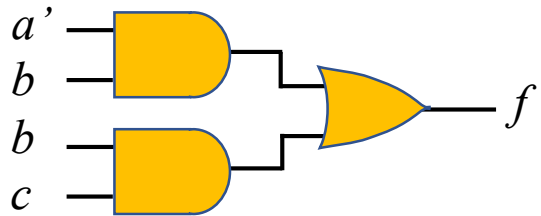

$$g(a, b, c) = ab' + ac$$

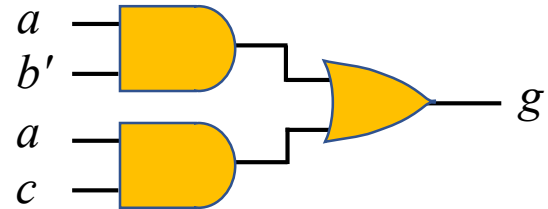

12 gate inputs and 6 gates (how to reduce the cost?)

Multiple Output Problems

| c \ ab | 00 | 01 | 11 | 10 |
|--------|-------|-------|-------|-------|
| | m_0 | m_2 | m_6 | m_4 |
| 0 | m_0 | m_2 | m_6 | m_4 |
| 1 | m_1 | m_3 | m_7 | m_5 |

$$f(a, b, c) = \sum m(2, 3, 7)$$

| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| | | | | |
| 0 | | 1 | | |
| 1 | | 1 | 1 | |

$$f(a, b, c) = a'b + bc$$

$$g(a, b, c) = \sum m(4, 5, 7)$$

| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| | | | | |
| 0 | | | | 1 |
| 1 | | | 1 | 1 |

$$g(a, b, c) = ab' + ac$$

Multiple Output Problems

| c \ ab | 00 | 01 | 11 | 10 |
|--------|-------|-------|-------|-------|
| | m_0 | m_2 | m_6 | m_4 |
| 0 | | | | |
| 1 | | | | |

$$f(a, b, c) = \sum m(2, 3, 7)$$

| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| | | | | |
| 0 | | 1 | | |
| 1 | | 1 | 1 | |

$$f(a, b, c) = a'b + abc$$

$$g(a, b, c) = \sum m(4, 5, 7)$$


| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| | | | | |
| 0 | | | | 1 |
| 1 | | | 1 | 1 |

$$g(a, b, c) = ab' + abc$$

Multiple Output Problems

$$f(a, b, c) = a'b + abc$$

$$g(a, b, c) = ab' + abc$$

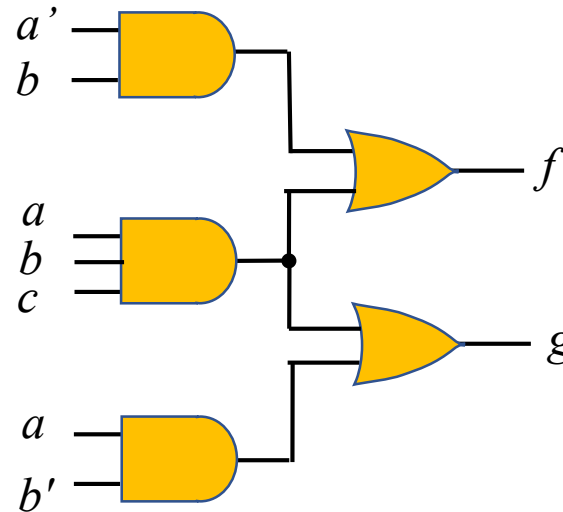

11 gate inputs and 5 gates!!!

Multiple Output Problems

$$f(a, b, c) = \sum m(2, 3, 7)$$

$$g(a, b, c) = \sum m(4, 5, 7)$$

- fg : mark as '-' when exist in respective function, else '0'.
- Terms can be combined when they have a common '-'
- After combination, any tag with a '0' will be '0', else '-'.
- Terms are marked if they are covered by the combined terms.

| Minterms | abc |
|----------|-------|
| m_0 | 000 |
| m_1 | 001 |
| m_2 | 010 |
| m_4 | 100 |
| m_3 | 011 |
| m_5 | 101 |
| m_6 | 110 |
| m_7 | 111 |

| Minterms | $abc \ fg$ |
|----------|------------|
| m_2 | 010 -0 ✓ |
| m_4 | 100 0- ✓ |
| m_3 | 011 -0 ✓ |
| m_5 | 101 0- ✓ |
| m_7 | 111 -- |

| Minterms | $abc \ fg$ |
|------------|------------|
| m_2, m_3 | 01- -0 |
| m_4, m_5 | 10- 0- |
| m_3, m_7 | -11 -0 |
| m_5, m_7 | 1-1 0- |

Multiple Output Problems

| Minterms | <i>abc fg</i> | |
|------------|---------------|--|
| m_2 | 010 -0 ✓ | PI_1 PI_2 PI_3 PI_4 PI_5 |
| m_4 | 100 0- ✓ | |
| m_3 | 011 -0 ✓ | |
| m_5 | 101 0- ✓ | |
| m_7 | 111 -- | |
| Minterms | <i>abc fg</i> | |
| m_2, m_3 | 01- -0 | |
| m_4, m_5 | 10- 0- | |
| m_3, m_7 | -11 -0 | |
| m_5, m_7 | 1-1 0- | |

| PI | Minterms | <i>abc</i> | <i>fg</i> | <i>f</i> | | | <i>g</i> | | |
|--------|------------|------------|-----------|----------|---|---|----------|---|---|
| | | | | 2 | 3 | 7 | 4 | 5 | 7 |
| PI_1 | m_7 | 111 | -- | | | x | | | x |
| PI_2 | m_2, m_3 | 01- | -0 | x | x | | | | |
| PI_3 | m_4, m_5 | 10- | 0- | | | | x | x | |
| PI_4 | m_3, m_7 | -11 | -0 | | x | x | | | |
| PI_5 | m_5, m_7 | 1-1 | 0- | | | | | x | x |


Multiple Output Problems

| PI | Minterms | abc | fg | f | | | g | | |
|--------|------------|-------|------|-----|---|---|-----|---|---|
| | | | | 2 | 3 | 7 | 4 | 5 | 7 |
| PI_1 | m_7 | 111 | -- | | | x | | | x |
| PI_2 | m_2, m_3 | 01- | -0 | x | x | | | | |
| PI_3 | m_4, m_5 | 10- | 0- | | | | x | x | |
| PI_4 | m_3, m_7 | -11 | -0 | | x | x | | | |
| PI_5 | m_5, m_7 | 1-1 | 0- | | | | | x | x |

| PI | Minterms | abc | fg | f | g |
|--------|------------|-------|------|-----|-----|
| | | | | 7 | 7 |
| PI_1 | m_7 | 111 | -- | x | x |
| PI_4 | m_3, m_7 | -11 | -0 | x | |
| PI_5 | m_5, m_7 | 1-1 | 0- | | x |

$$f(a, b, c) = PI_1 + PI_2 = abc + a'b$$

$$g(a, b, c) = PI_1 + PI_3 = abc + ab'$$

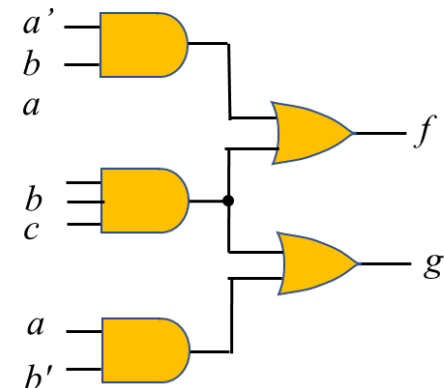

Exercise

Reduce the following functions that will use the least number of gates and gate inputs.

$f(a, b, c, d)$

| $cd \backslash ab$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | 1 | 1 | | 1 |
| 01 | 1 | 1 | | 1 |
| 11 | | | | |
| 10 | 1 | 1 | | |

$g(a, b, c, d)$

| $cd \backslash ab$ | 00 | 01 | 11 | 10 |
|--------------------|----|----|----|----|
| 00 | | | | 1 |
| 01 | | | | 1 |
| 11 | | | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 |