
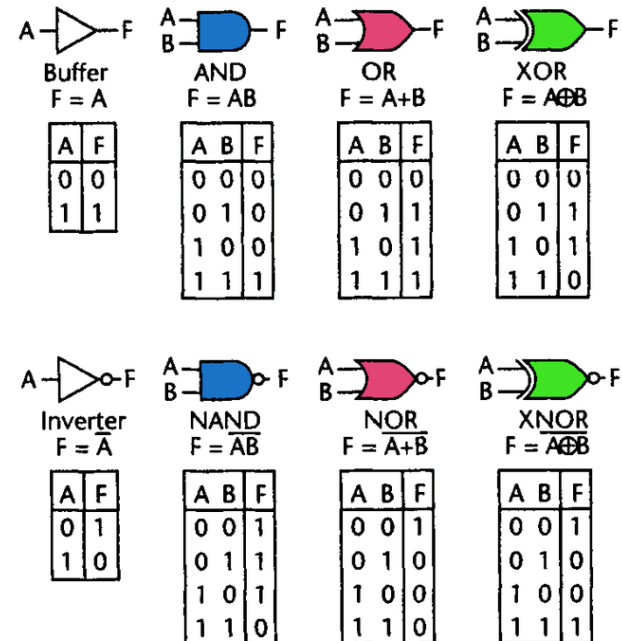


EE2000 Logic Circuit Design

Lecture 1 – Solution for Exercises


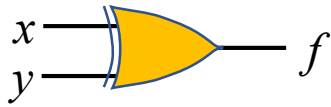


Exercises




x	y	f
0	0	0
1	0	1
0	1	1
1	1	0

$$f = xy' + x'y$$

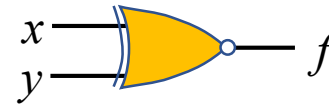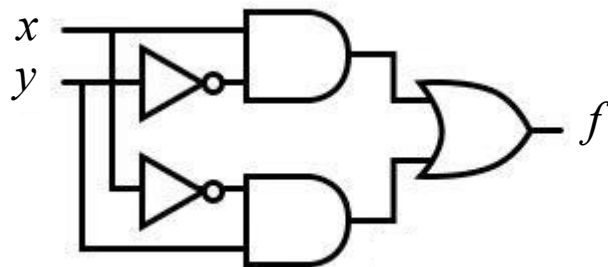

x	y	f
0	0	1
1	0	0
0	1	0
1	1	1


$$f = x'y' + xy$$

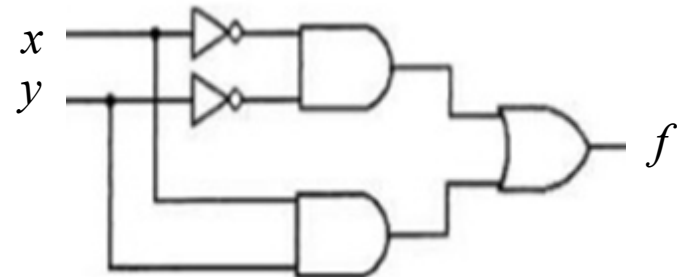

Exercises

Given the Boolean function $f(x, y, z) = xy' + x'z'$, draw the Logic Circuit and work out the truth table.

x	y	z	xy'	$x'z'$	$xy' + x'z'$
0	0	0	0	1	1
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	0	0	0

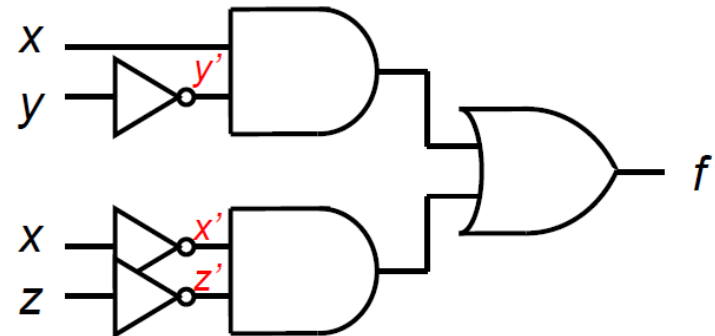

Question

- Which of the following has the same function as $x + x'y$?

a) $x + xy'$

b) $x + y$

c) $x' + y$

d) y

$$\begin{aligned}x + x'y &= (x + x')(x + y) && \text{distributive} \\ &= 1 \cdot (x + y) && \text{complement} \\ &= x + y && \text{identity}\end{aligned}$$

Exercise

- Simplify the following expression.

$$xyz' + xyz + xy'z + x'yz + x'y'z + x'y'z'$$

$$= xy(z' + z) + xy'z + x'yz + x'y'(z + z') \text{ complement}$$

$$= xy + xy'z + x'yz + x'y'$$

$$= x(y + y'z) + x'(y' + yz) \text{ simplification}$$

$$= x(y + z) + x'(y' + z)$$

$$= xy + x'y' + z(x + x') \text{ complement}$$

$$= xy + x'y' + z$$

5 literals; 3 terms

Exercise


- Simplify the following expression.

$$(x + y + z)(x + y + z')(x + y' + z)(x + y' + z') \quad \text{adjacency}$$

$$= (x + y)(x + y') = x$$

1 literal; 1 term

Exercise

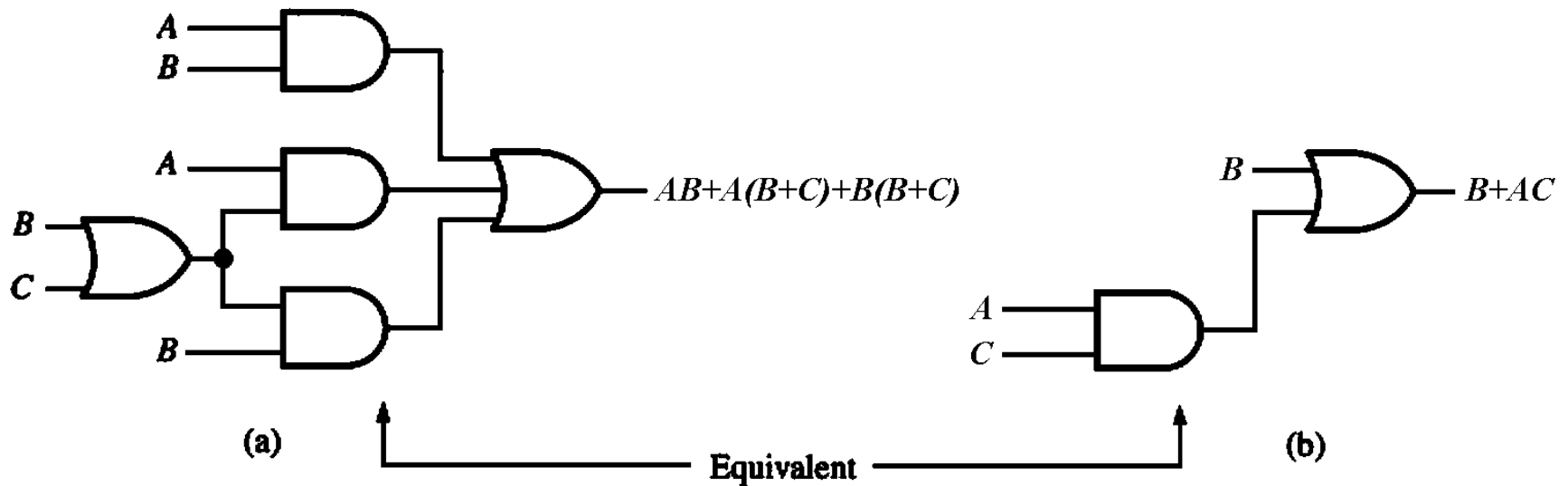

Prove that the above Circuit (a) is equivalent to Circuit (b).

Solution by Boolean Algebra Simplification

$$AB + A(B + C) + B(B + C)$$

$$AB + AB + AC + BB + BC$$

$$AB + AB + AC + B + BC$$

$$AB + AC + B + BC$$

$$AB + AC + B$$

$$B + AC$$

$$BB=B$$

$$AB+AB=AB$$

$$B+BC=B$$

$$AB+B=B$$

Idempotent

Idempotent

Absorption

Absorption

Exercise


$$\begin{aligned}f(w, x, y, z) &= wxy' + w'y'z + wx'y' + xy'z + w'z \\&= wxy' + wx'y' + xy'z + w'z && \text{adsorption} \\&= wy' + w'z + xy'z && \text{adjacency}\end{aligned}$$

Term 1	Term 2	Consensus Term
wy'	$w'z$	$y'z$

$$\begin{aligned}&= wy' + w'z + xy'z + y'z && \text{Add the consensus term} \\&= wy' + w'z + y'z && \text{adsorption} \\&= wy' + w'z && \text{Remove the consensus term}\end{aligned}$$

Exercise

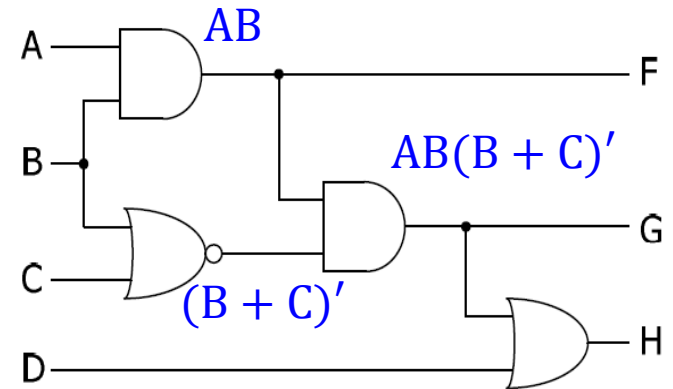1. Derive the Boolean functions to describe the operations of the logic circuit as shown.
2. Simplify the functions and draw the circuit.



$$F = AB$$

$$\begin{aligned} G &= AB(B + C)' \\ &= ABB'C' \quad \text{deMorgan} \\ &= 0 \quad \text{Complement} \end{aligned}$$

$$H = AB(B + C)' + D = D$$

