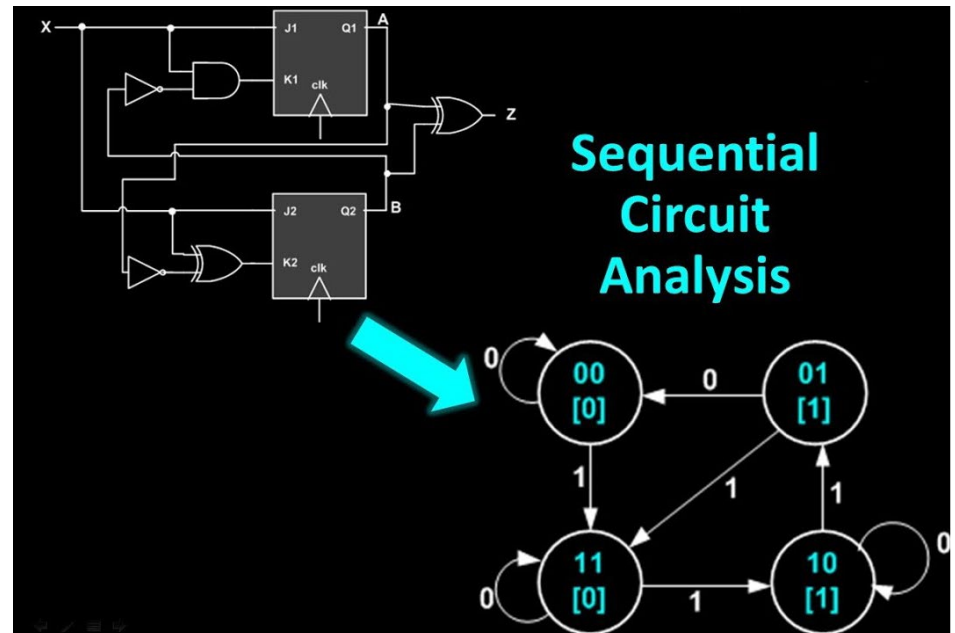



EE2000 Logic Circuit Design

Lecture 9 – Sequential Logic Circuit Design




Examples (Mealy or Moore?)

(a)

 


None

(b)

 

Moore


(c)

 


Mealy

Other FFs


State diagram

 

D-FF

 

JK-FF

 

T-FF

Characteristic equation

$$Q_t^* = D$$

$Q_t^* = JQ_t' + K'Q_t$

$Q_t^* \backslash Q_t$	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$Q_t^* = T \oplus Q_t$

$Q_t^* \backslash Q_t$	0	1
0		1
1	1	

Example (Sequence Detector)

Design a Moore machine to detect the sequence “111”
(Overlapping)

In other words,

Design a system with one input x and one output z such that $z = 1$ if x has been 1 for at least three consecutive clock times.

x	0	1	1	0	1	1	1	0	1	1	1	1	1	0
z	0	0	0	0	0	0	0	1	0	0	0	1	1	1

Question: How about no overlapping is allowed?

x	1	1	1	1	1	0
z	0	0	0	1	0	0

Example (Sequence Detector)

x	0	1	1	0	1	1	1	0	1	1	1	1	1	0
z	0	0	0	0	0	0	0	1	0	0	0	1	1	1

STEP 1: Determine what needs to be stored in memory and how to store them.

A: Input is '0'

B: one '1' is detected

C: two '1's are detected

D: three '1's are detected and output 1

Example (Sequence Detector)

STEP 2: Work out the State Diagram

x	1	1	1	1	1	1	0
z	0	0	0	1	0	0	1


A: Input is '0'

B: one '1' is detected


C: two '1's are detected

D: three '1's are detected and output 1

 Question: How can we change the diagram if no overlapping is allowed?




Exercise

 

$$Q_1^* = D_1 = Q_1 Q_2 + x Q_1'$$

$$Q_2^* = D_2 = Q_1' Q_2' + x Q_1$$

Present State $Q_1 \ Q_2$	Input X	
	0	1
(0 0)	(0 1)	(1 1)
(0 1)	(0 0)	(1 0)
(1 0)	(0 0)	(0 1)
(1 1)	(1 0)	(1 1)

 

Exercise (Sequence Detector)

Design a Mealy machine to detect the sequence “111”
(Overlapping)

In other words,

Design a system with one input x and one output z such that $z = 1$ if x has been 1 for at least three consecutive clock times.

x	0	1	1	0	1	1	1	0	1	1	1	1	1	0
z	0	0	0	0	0	0	1	0	0	0	1	1	1	0

Exercise (Sequence Detector)

x	0	1	1	0	1	1	1	0	1	1	1	1	1	0
z	0	0	0	0	0	0	1	0	0	0	1	1	1	0

STEP 1: Determine what needs to be stored in memory and how to store them.

A: input is '0' *if next input is 0, remains at A else B

B: one '1' is detected *if next input is 0, back to A else C

C: two '1's are detected

 * if next input is 0, back to A and output '0',
else remains at C and output '1'

Exercise (Sequence Detector)


STEP 2: Work out the State Diagram

A: Input is '0' *if next input is 0, remains at A else B

B: one '1' is detected *if next input is 0, back to A else C

C: two '1's are detected

 
* if next input is 0, back to A and output '0',
else remains at C and output '1'



 Exercise (Sequence Detector)

STEP 3: Work out the analysis table with assigned FFs

3 states \rightarrow 2 FFs (We use D-FFs in this example)



Assign State A:

$Q_1 \rightarrow 0$ and $Q_2 \rightarrow 0$ etc

Present State ($Q_1 Q_2$)	Input X	Next stage		Present Output Z
		Q_1^*	Q_2^*	
A (0 0)	0	0	0	0
A (0 0)	1	0	1	0
B (0 1)	0	0	0	0
B (0 1)	1	1	1	0
(1 0)	x	x	x	x
C (1 1)	0	0	0	0
C (1 1)	1	1	1	1

Exercise (Sequence Detector)

STEP 4: Work out D_1 and D_2

Present State (Q_1Q_2)	Input X	Next stage $Q_1^* \quad Q_2^*$		Present Output Z
A (0 0)	0	0	0	0
A (0 0)	1	0	1	0
B (0 1)	0	0	0	0
B (0 1)	1	1	1	0
(1 0)	x	x	x	x
C (1 1)	0	0	0	0
C (1 1)	1	1	1	1

Q_1^*

		Q_1Q_2			
		00	01	11	10
x	0	0	0	0	x
	1	0	1	1	x

$$D_1 = Q_1^* = xQ_2$$

Q_2^*

		Q_1Q_2			
		00	01	11	10
x	0	0	0	0	x
	1	1	1	1	x

$$D_2 = Q_2^* = x$$

Exercise (Sequence Detector)

STEP 5: Work out z

Present State (Q_1Q_2)	Input X	Next stage $Q_1^* \quad Q_2^*$		Present Output Z
A (0 0)	0	0	0	0
A (0 0)	1	0	1	0
B (0 1)	0	0	0	0
B (0 1)	1	1	1	0
(1 0)	x	x	x	x
C (1 1)	0	0	0	0
C (1 1)	1	1	1	1

Truth table for output z based on inputs x and state Q_1Q_2 :

		Q_1Q_2			
		00	01	11	10
x	0	0	0	0	x
	1	0	0	1	x

Note: The output $z=1$ for the state $(Q_1, Q_2) = (1, 1)$ when $x=1$ is circled in blue.

$$z = xQ_1$$


Exercise (Sequence Detector)

STEP 6: Draw the sequential logic circuits

$$D_1 = xQ_2$$

$$D_2 = x$$

$$z = xQ_1$$

 

Exercise (Sequence Detector)

Use T FFs to design a Mealy machine to detect the sequence “111” (Overlapping)

Present State ($Q_1 Q_2$)	Input X	Next stage		Flip-Flops		Present Output Z
		Q_1^*	Q_2^*	T_1	T_2	
A (0 0)	0	0	0			0
A (0 0)	1	0	1			0
B (0 1)	0	0	0			0
B (0 1)	1	1	1			0
(1 0)	x	x	x			x
C (1 1)	0	0	0			0
C (1 1)	1	1	1			1

T	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	Q_t	$\overline{Q_t}$	Hold
1	$\overline{Q_t}$	Q_t	Toggle

Exercise (Sequence Detector)

Use T FFs to design a Mealy machine to detect the sequence “111” (Overlapping)

Present State ($Q_1 Q_2$)	Input X	Next stage		Flip-Flops		Present Output Z
		Q_1^*	Q_2^*	T_1	T_2	
A (0 0)	0	0	0	0	0	0
A (0 0)	1	0	1	0	1	0
B (0 1)	0	0	0	0	1	0
B (0 1)	1	1	1	1	0	0
(1 0)	x	x	x	x	x	x
C (1 1)	0	0	0	1	1	0
C (1 1)	1	1	1	0	0	1

T	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	Q_t	$\overline{Q_t}$	Hold
1	$\overline{Q_t}$	Q_t	Toggle

Exercise (Sequence Detector)

Present State (Q_1Q_2)	Input X	Flip-Flops	
		T_1	T_2
A (0 0)	0	0	0
A (0 0)	1	0	1
B (0 1)	0	0	1
B (0 1)	1	1	0
(1 0)	x	x	x
C (1 1)	0	1	1
C (1 1)	1	0	0

T_1

x	Q_1Q_2			
	00	01	11	10
0	0	0	1	x
1	0	1	0	x

$$T_1 = xQ_1'Q_2 + x'Q_1$$




T_2

x	Q_1Q_2			
	00	01	11	10
0	0	1	1	x
1	1	0	0	x

$$T_2 = xQ_2' + x'Q_2$$

Exercise (Timing Diagram)

$$z = xQ_1$$

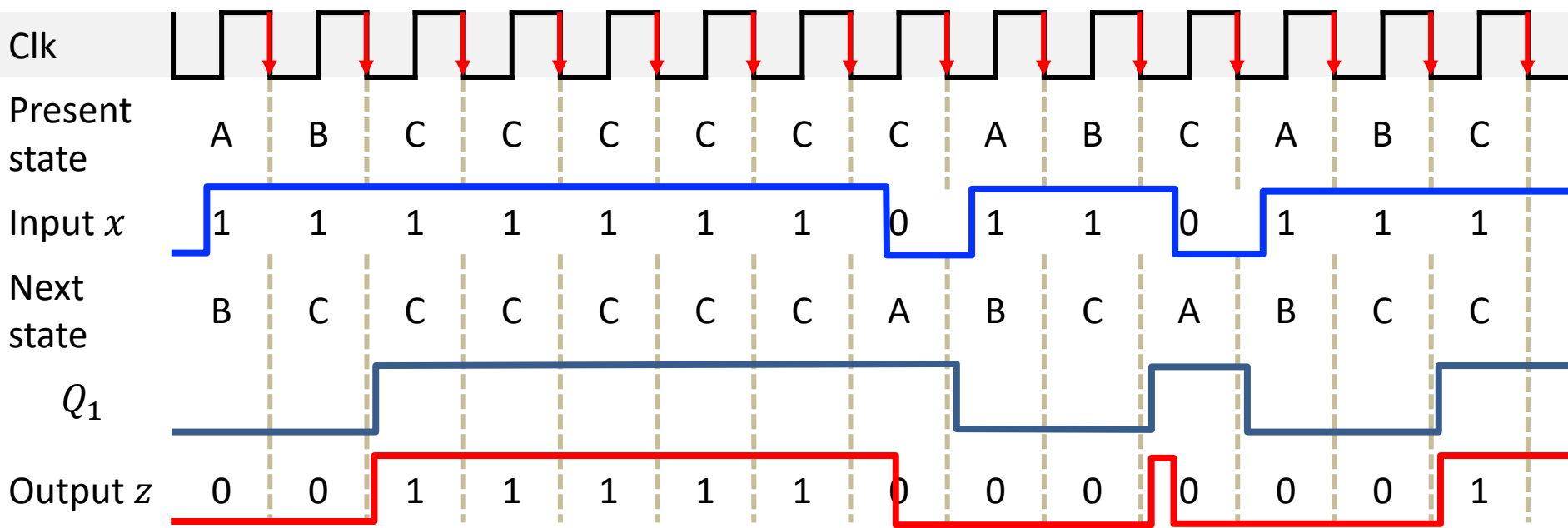  

Exercise

Present State	Input X		Present Output Z
	0	1	
A	I	C	0
B	B	I	0
C	C	G	0
D	I	C	1
E	D	E	1
F	I	C	1
G	E	F	1
H	H	A	0
I	A	C	0

Reduce the state table using partitioning method

$$P_0 = (A\ B\ C\ D\ E\ F\ G\ H\ I)$$

Group states based on same output

Exercise

Present State	Input X		Present Output Z
	0	1	
A	I	C	0
B	B	I	0
C	C	G	0
H	H	A	0
I	A	C	0
D	I	C	1
E	D	E	1
F	I	C	1
G	E	F	1

Reduce the state table using partitioning method

$$P_1 = (A\ B\ C\ H\ I)(D\ E\ F\ G)$$

A B C H I → Output 0

D E F G → Output 1

Exercise

Present State	Input <i>X</i>		Present Output <i>Z</i>
	0	1	
A	I	C	0
B	B	I	0
H	H	A	0
I	A	C	0
C	C	G	0
D	I	C	1
F	I	C	1
E	D	E	1
G	E	F	1

Reduce the state table using partitioning method

$$P_2 = (A\ B\ H\ I)(C)(D\ F)(E\ G)$$

Exercise

Present State	Input X		Present Output Z
	0	1	
A	I	C	0
I	A	C	0
B	B	I	0
H	H	A	0
C	C	G	0
D	I	C	1
F	I	C	1
E	D	E	1
G	E	F	1

Reduce the state table using partitioning method

$$P_3 = (A\ I)(B\ H)(C)(D\ F)(E)(G)$$

Exercise

Present State	Input <i>X</i>		Present Output <i>Z</i>
	0	1	
A = I	A	C	0
B = H	B	A	0
C	C	G	0
D = F	A	C	1
E	D	E	1
G	E	D	1

Reduce the state table using partitioning method

$$P_3 = (A\ I)(B\ H)(C)(D\ F)(E)(G)$$