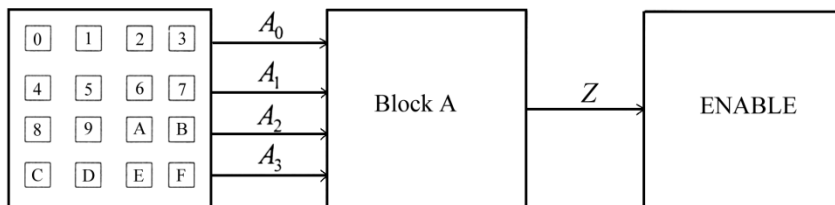


**EE 2000 Logic Circuit Design**  
**Semester B 2022/23**


Tutorial 1

1. Simplify the following expressions using boolean algebra
  - (a)  $f(w, x, y, z) = xy + \bar{w}\bar{y}z + \bar{w}x\bar{y} + wxy\bar{z} + \bar{w}yz + wz$
  - (b)  $f(x, y, z) = (x + y + z)(x + y + \bar{z})(x + \bar{y} + z)(x + \bar{y} + \bar{z})$
  - (c)  $f(a, b, c, d) = ab + bcd + ab'c' + abd + bc + abc'$
  - (d)  $f(a, b, c) = (a + b + c)(a + \bar{b} + c)(a + \bar{b} + \bar{c})(\bar{a} + \bar{b} + \bar{c})$
  
2. Given a function  $f(x, y, z) = \sum m(0, 2, 4, 6)$ 
  - (a) Show the truth table.
  - (b) Show the algebraic expression in standard SOP form.
  - (c) Show the minimum SOP expression and draw the circuit diagram.
  - (d) Show the algebraic expression in standard POS form.
  - (e) Show the minimum POS expression.
  
3. A simple locker system that has an output signal  $Z = 1$  when the hexadecimal keypad input is either 0, 1, 2, 3, 7, 8, 9, A or E; otherwise  $Z = 0$ . Assume that  $A_3 A_2 A_1 A_0$  represent a 4-digit binary number output from the keypad ( $A_3$  as the MSB). Block A decodes these signals and outputs the signal  $Z$ .



- (a) Write down the truth table of Block A.
- (b) Find the SOP and POS expression of Block A.
- (c) Design the circuit of Block A using minimum number of 2-input AND, OR gates and NOT gates.

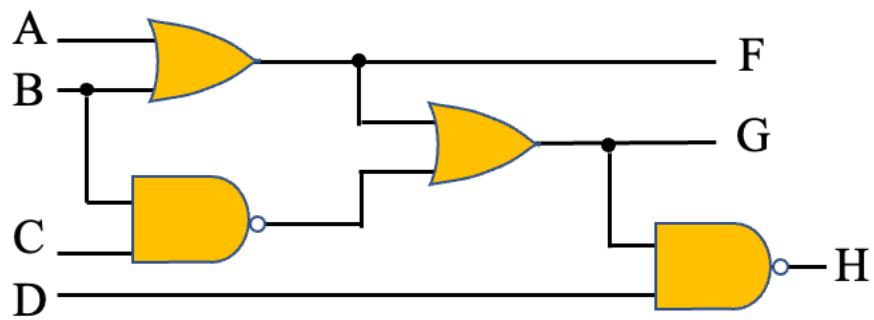4. (a) Derive Boolean functions to describe the operations of the combinational circuit as follow:



- (b) Hence, simplify and draw a new logic circuit.
- (c) Redraw the logic circuit with only 2-input NAND gates.