

**EE 2000 Logic Circuit Design  
Semester B 2023/24**

**Assignment 1**

**The solutions must be handwritten (20% deduction if not), scanned and uploaded to CANVAS by 23:59 hours, Feb 7, 2024.** Please do not use iPad to write the solution – treat this as practice for your examination and write on paper. **Please write your name and student No on the top of each answer sheet.**

1. Simplify the following logic expression using Boolean algebra. (15 marks)

$$F = \overline{wx} \cdot \overline{\overline{y} + z} \cdot \overline{wxy + z}$$

2. Use K-map to find all of the minimum SOP expressions and all of the minimum POS expressions of the following function. If there is more than one solution, label the solutions  $f_1, f_2, \dots$

$$f(w, x, y, z) = \Sigma m(0, 1, 3, 5, 7, 8, 14) + \Sigma d(2, 12, 15) \quad (41 \text{ marks})$$

3. Use Quine-McCluskey method to find all of the minimum SOP expressions of the following function. If there is more than one solution, label the solutions  $f_1, f_2, \dots$

$$f(w, x, y, z) = \Sigma m(1, 3, 4, 7, 13, 15) + \Sigma d(0, 5, 6, 8, 12) \quad (44 \text{ marks})$$