 



EE 2000 Logic Circuit Design
Semester B 2023/24

Tutorial 7



- The waveforms are applied to the inputs of an SN7476 *JK* flip-flop (negative-edge triggered). Complete the timing diagram by drawing the waveforms of flip-flop output *Q*.



 - The circuit contains a *D* latch, a positive-edge-triggered *D* flip-flop, and a negative edge-triggered *D* flip-flop. Complete the timing diagram for the waveform of signals y_1 , y_2 and y_3 .



 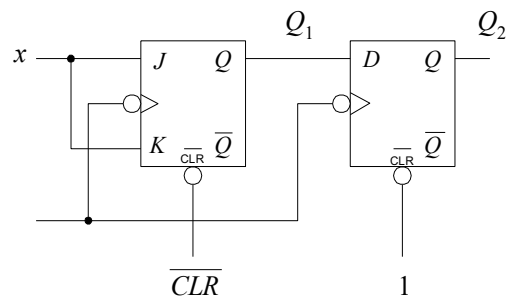3. The circuit contains a negative edge-triggered JK flip-flop and a D flip-flop. Complete the timing diagram by drawing the waveforms of signals Q_1 and Q_2 .



4. Complete the timing diagram by drawing the waveforms of signals q_1 and q_2 .

