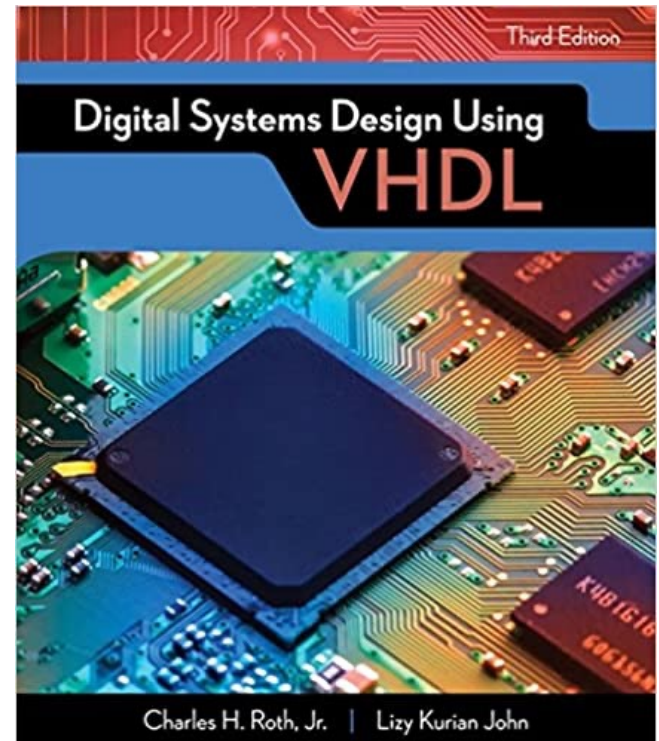


# EE2000 Logic Circuit Design

---

## Lecture 4- VHDL




# Outline

- 4.1 Hardware Description Language (HDL)
- 4.2 VHDL Code Structure
- 4.3 VHDL Data Types
- 4.4 VHDL Operators
- 4.5 VHDL Syntax for Logic Circuits

# 4.1 Hardware Description Language

- Hardware Description Languages (HDLs) is a software programming language used to **describe a digital system**
- Behavioral description: The general function of the design at the **algorithmic level** without specifying physical components, gates, *etc.*
- Structural description: **Specific components, gates, and their interconnections** are associated with the design

# Modern Digital System Design Flow

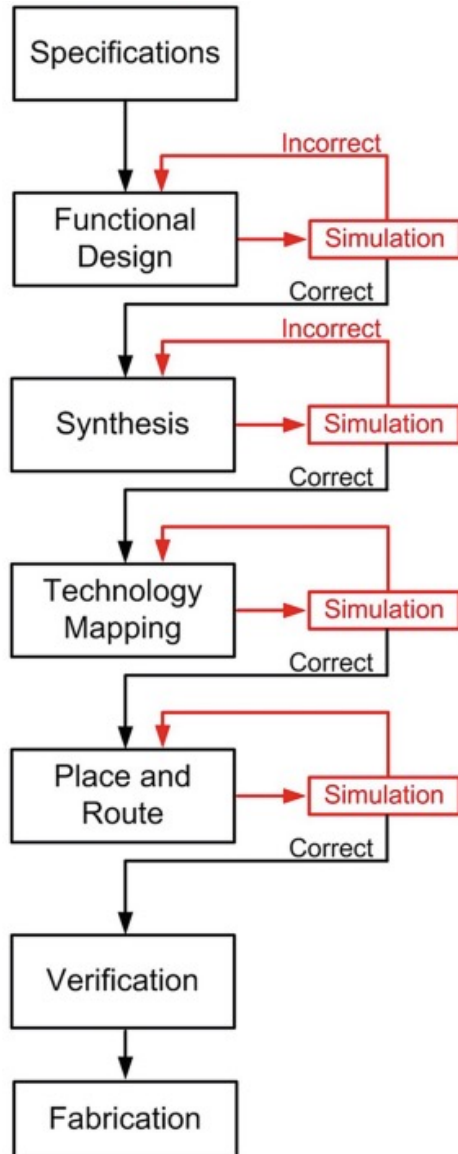

State the desired behavior of the design

Design the system using HDL. The design is simulated to verify its functionality

Convert the design in HDL to gate-level connection

Map design to specific logic technology (physical components)

Arrange components to minimize area needed, wiring length and crossings


Final design is analyzed (gate and propagation delays, power consumption, etc.)

FPGA, ASIC, board-level, discrete parts

# VHDL


- Two popular HDLs (IEEE standard)
  - Verilog: [Verifying Logic](#)
  - VHDL: [Very High Speed Integrated Circuit HDL](#)
- In this lecture, we learn VHDL
- In the lab, we use Vivado design tool from Xilinx to design, simulate and synthesize the logic circuit/system
- A top-down design methodology: System is specified and tested using simulator; then refined to structural description and led to actual hardware implementation

## 4.2 VHDL Code Structure

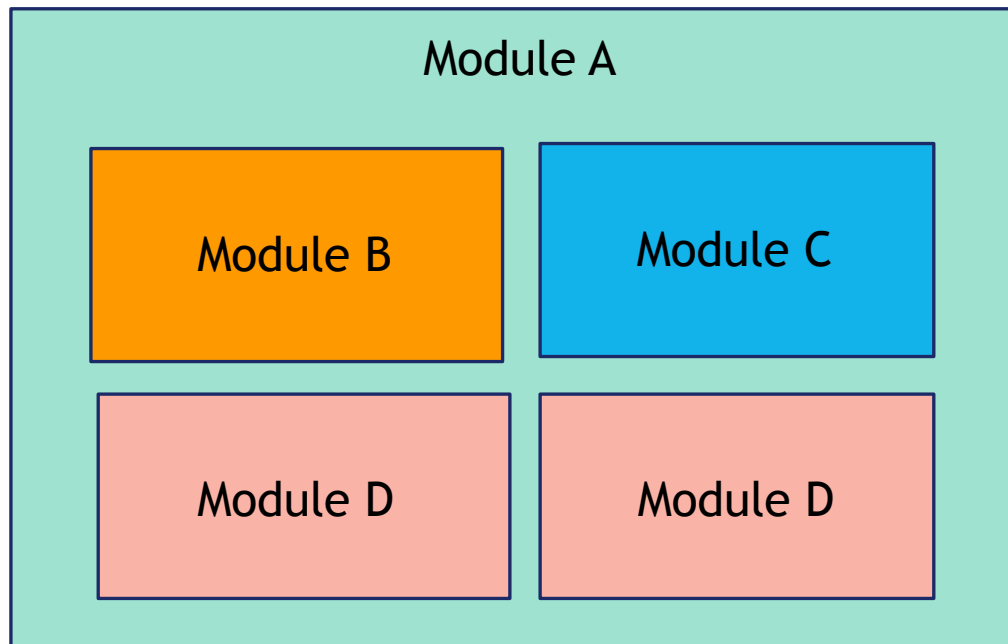

- Like breaking down complicated circuits into various smaller circuits
- Each module describes a **smaller circuit**
- Modules are connected through **ports (inputs/outputs)** to form the final circuit

# VHDL Code Structure - Illustration

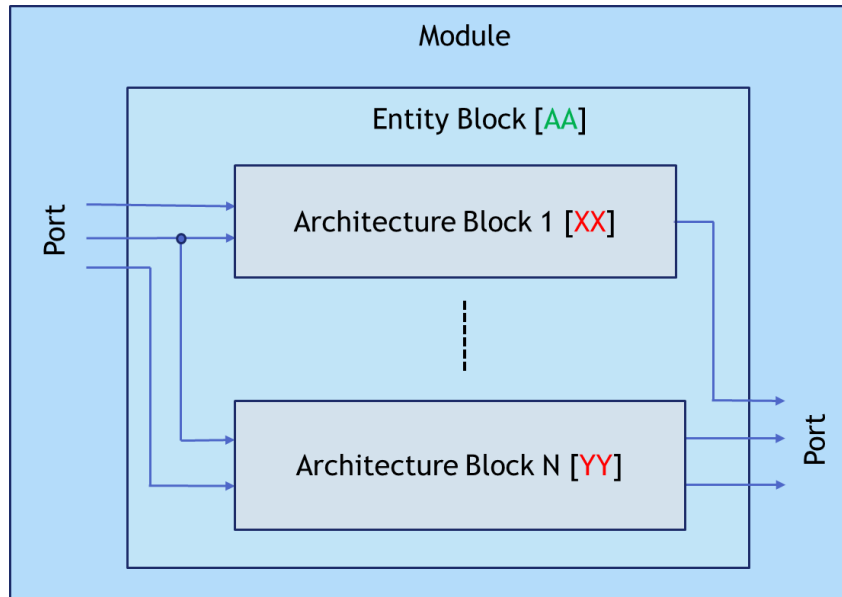

**Library declaration**

**Entity declaration**


**Architecture  
declaration**

**Library declaration:** IEEE Standard library, e.g., STD\_LOGIC\_1164 contains STD\_LOGIC types & related functions

**Entity declaration:** defines the input or output ports to the current module

**Architecture declaration:** describes the logic function of the corresponding entity

# VHDL Format and Synthax

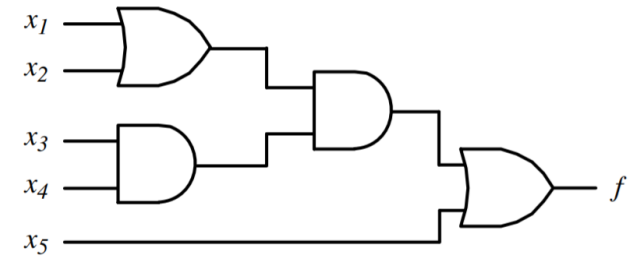

Library declaration	<pre>library IEEE; use IEEE.std_logic_1164.all;</pre>	<pre>-- load to access a library -- use a package in the library</pre>
Entity declaration	<pre>entity logic_c is     port (x1, x2, x3, x4, x5 : in bit;           f: out bit); end logic_c;</pre>	<pre>-- define the name of the entity -- inputs and data type -- outputs and data type</pre>
Architecture declaration	<pre>architecture behavior of logic_c is begin     f &lt;= ((x1 or x2) and           (x3 and x4)) or x5); end behavior;</pre>	<pre>-- define the architecture and -- specify the entity --define the logic operation</pre>



# Entity Synthax

```
entity entity-name is  
    port (interface-signal-declaration);  
end entity-name;
```

Interface-signal-declaration

```
list-of-signals: mode data-type := initial value;
```

Example

```
port (A, B: in integer := 2; C, D: out bit );
```

- A and B are input signals of type integer that are initially set to 2
- C and D are output signals of type bit (default '0')

# Entity Synthax

**entity** `two_gates` **is**

**port** (`A, B`: **in** integer := 2; `C, D`: **out** bit );

**end** `two_gates`;

- Port name and entity name (identifiers)
  - may contain letters, numbers and underscore character (`_`)
  - Must start with a letter
  - Cannot end with underscore or use double underscores
- Mode: **in**, **out**, **inout**, **buffer** (output + feedback)
- VHDL is case **insensitive**!
  - `CLK <= A and B`
  - `Clk <= a AND b`

# Question

Which of the following identifier is illegal to be used as an entity name in VHDL?

- TwO\_gaTE
- 2\_gate
- T2-gate
- \_2gate
- AND

# Data Objects

**Data objects:** A container for data values; a place to store and retrieve data values

## **Constant:**

- Hold unchangeable values
- Can be declared anywhere that allows declaration
- Declaration syntax

**constant** *name*: *data\_type* := *initial value*;

e.g. **constant** *data\_bus*: *integer* := 4 ns;

# Data Objects

## Signal:

- Represent **wires** in schematics
- Declare in **port** of **entity** as inputs/outputs
- Declare in **architecture** before **begin** as internal signals
- Declaration synthax (without/with initial value)

**signal** *name*: *data\_type* := *initial value*;

e.g. **signal** *count*: *bit* := '1';

**signal** *count*: *bit*;


- Assignment synthax

*count* <= '0';

```
entity AA is  
  port (x1, x2, x3, x4, x5 : in bit;  
        f: out bit);  
end AA;
```

```
architecture AA of BB is  
  signal count: bit := '1';  
begin  
  count <= '0';  
end AA;
```

# Architecture declaration

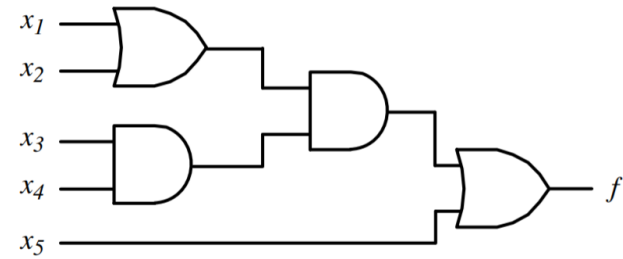


Version 1

```
architecture behavior of logic_c is -- define the architecture
begin
    f <= ((x1 or x2) and           --define the logic operation
          (x3 and x4)) or x5);
end behavior;
```

Version 2

```
architecture behavior of logic_c is -- define the architecture
signal y1, y2, y3: bit;             -- declare internal signals
begin
    y1 <= x1 or x2;
    y2 <= x3 and x4;
    y3 <= y1 and y2;
    f <= y3 or x5;                   --define the logic operation
end behavior;
```

# 4.3 VHDL Data Types

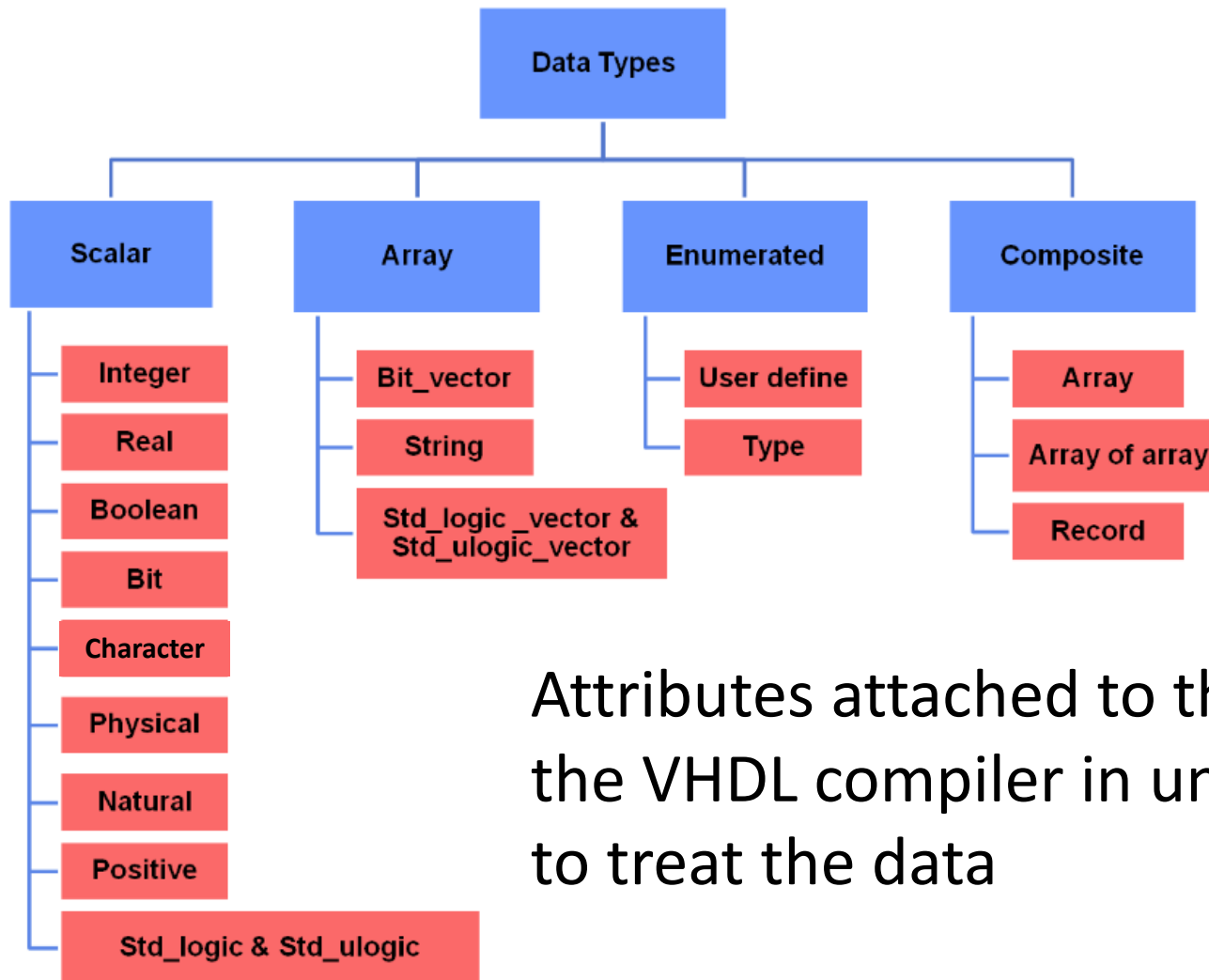

Attributes attached to the data that help the VHDL compiler in understanding how to treat the data

# Standard Data Types

Type	Description
Boolean	FALSE or TRUE
Bit	0 or 1
Character	Any ASCII character
Integer	Integer in the range $-2^{31}$ to $+(2^{31} - 1)$
Natural	Integer in the range 0 to $+(2^{31} - 1)$
Positive	Integer in the range 1 to $+(2^{31} - 1)$
Real	Floating-point number in the range $-1.0\text{E}38$ to $+1.0\text{E}38$
Time	An integer with units fs, ps, ns, us, ms, sec, min, or hr



# Bit & Bit Vector

Signal declaration synthax

**signal** *name*: *type*;

## Examples

**signal** *x1*: *bit*;

**signal** *y1*: *integer* := 1;

**signal** *z1*: *real* := 3.14159;

**signal** *x1*: *bit\_vector*(3 downto 0);

**signal** *x1*: *bit\_vector*(0 to 3);

**bit**: a bit object with value either '0' or '1'

**bit\_vector**: multi-bit data in an array of bit objects

# Bit Vector

**signal** **x1**: **bit\_vector(3 downto 0)**;

- Elements: x1(3), x1(2), x1(1), x1(0)
- x1(3) holds the most significant bit
- x1 <= "0101";
- x1(3) = '0', x1(2) = '1', x1(1) = '0', x1(0) = '1'

**signal** **x1**: **bit\_vector(0 to 3)**;

- Elements: x1(0), x1(1), x1(2), x1(3)
- x1(0) holds the most significant bit
- x1 <= "0101";
- x1(0) = '0', x1(1) = '1', x1(2) = '0', x1(3) = '1'

# Bit Vector Assignment Types

**signal** x: bit\_vector(3 **downto** 0) **:=** "0000";

- x **<=** "0101";
  - x(3) = '0', x(2) = '1', x(1) = '0', x(0) = '1'
- x(3) <= '1';
  - x(3) = '1', x(2) = '0', x(1) = '0', x(0) = '0'
- x <= (0 | 1 => '1', **others** => '0');
  - x(3) = '0', x(2) = '0', x(1) = '1', x(0) = '1'
- x <= (2 **downto** 0 => '1', **others** => '0');
  - x(3) = '0', x(2) = '1', x(1) = '1', x(0) = '1'

# Exercise

```
signal C: bit_vector (0 to 3);  
signal D: bit_vector (3 downto 0);  
signal A: bit_vector (7 downto 0);
```

```
C <= "1101";  
D <= C;  
A(6 downto 3) <= D;
```

Determine the stored value in the following bit object

```
C(0) =   C(1) =   C(2) =   C(3) =  
D(3) =   D(2) =   D(1) =   D(0) =  
A(6) =   A(5) =   A(4) =   A(3) =
```

# Array Data Type

## Bit Vector

- An array of bits
- **signal** str\_1: bit\_vector(1 to 3) := “0011”;

## String

- An array of character type elements
- **signal** str\_1: string(1 to 11) := “Welcome All”;

# Physical Data Type

- Physical type allows user to define **measurement units**, like length, time, pressure, capacity, etc.
- The only predefined physical type is **time**

**type time is range -2147483647 to 2147483647**

**units**

fs;

ps = 1000 fs;

ns = 1000 ps;

us = 1000 ns;

ms = 1000 us;

sec = 1000 ms;

min = 60 sec;

hr = 60 min;

**end units;**

**signal counter: time := 1 ns;**

**\* Note: Integer only**

# User Defined Physical Type

You can define your own physical type,

e.g. **type distance is range 0 to 1E7**

**units**

um; -- micrometer

mm = 1000 um; -- millimeter

cm = 10 mm; -- centimeter

m = 100 cm; -- meter

inch = 25400 um;

**end units;**

**signal** dis1, dis2: distance;

Dis1 <= 28 mm;

Dis2 <= 2 inch – 1 mm;

# User Defined Enumerated Data Type

- Predefined Enumeration types

- **type** BOOLEAN is (FALSE, TRUE);

- **type** BIT is ('0', '1');

- Define your own enumerated type,

e.g.

**type** colors is (RED, GREEN, BLUE);

**type** state is (S0, S1, S2, S4);

- Leftmost value is the least and is the default value

e.g. **when** my\_color >= RED



# User Defined Enumerated Data Type

- Subtype: Create a custom type from one of the existing types (a constrained version)

**subtype** integer\_8\_bit is integer **range** 0 to 255;

**subtype** MyBit is std\_logic **range** '0' to '1';

**signal** x1: integer\_8\_bit;


**signal** y1: MyBit;

\*Integer: in the range  $-2^{31}$  to  $+(2^{31} - 1)$

# IEEE std\_logic\_1164 package

- Bit only provides two outputs '0' or '1'
- We might need more states, such as don't care, uninitialized, etc.

e.g.

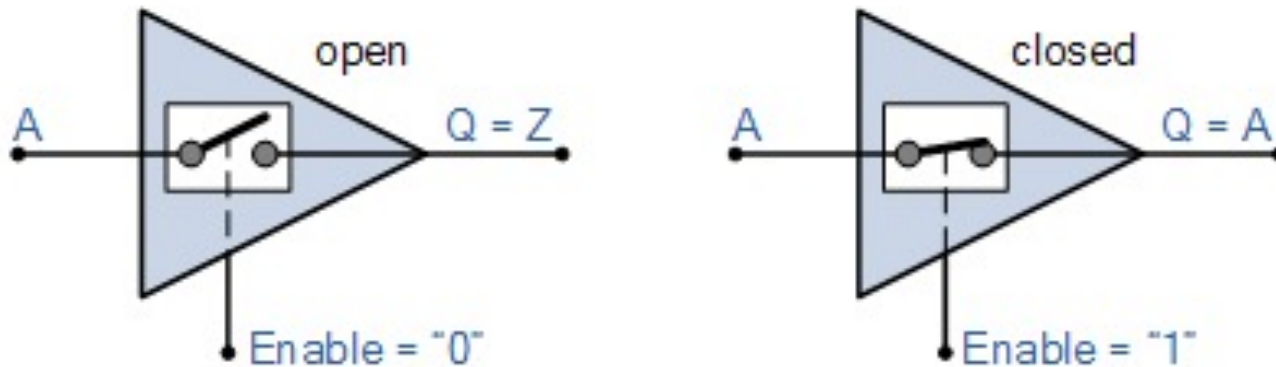

Tri-State buffer: When Enable is "0", the circuit is disabled, High-impedance (High-Z) state

# IEEE std\_logic\_1164 package

Type	Description
U	Uninitialized; Default value
X	Unknown. Cannot determine as 1 or 0
0	Logic 0
1	Logic 1
Z	High Impedance (Tri-state buffer when not enabled)
W	Weak signal, can't tell if it should be 0 or 1
L	Weak signal that should probably go to 0
H	Weak signal that should probably go to 1
-	Don't care

# std\_logic and std\_logic\_vector

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
signal x1: std_logic;
```


```
signal x2: std_logic;
```

```
signal x3: std_logic;
```

```
signal x4: std_logic;
```

```
signal x: std_logic_vector(0 to 3);
```

# User Defined Array Data Type

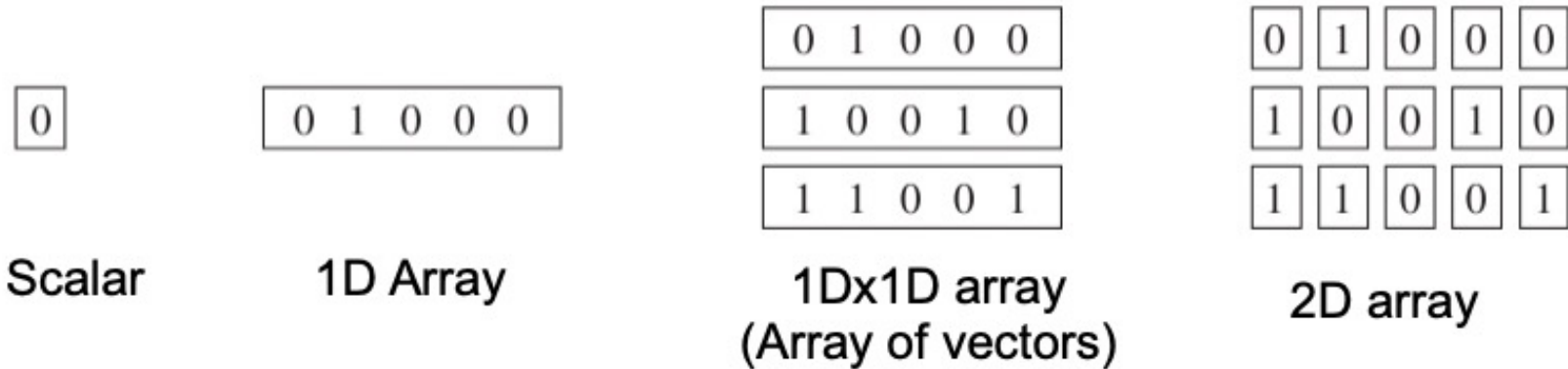

**type** `type_name` **is** **array** (`specification`) **of** `data_type`;  
**signal** `signal_name`: `type_name` := `initial_value`;

# User Defined Array Data Type

**type** row **is array** (7 **downto** 0) **of** std\_logic;

- Define a **1D array** named as **row** with eight STD\_LOGIC values

0	1	1	0	1	0	0	1
---	---	---	---	---	---	---	---

**type** array1 **is array** (0 **to** 3) **of** row;

- Define a **1D × 1D array** named as **array1** with 4 rows of vectors (eight STD\_LOGIC values)

0	1	1	0	1	0	0	1
---	---	---	---	---	---	---	---

0	1	1	0	1	0	0	1
---	---	---	---	---	---	---	---

0	1	1	0	1	0	0	1
---	---	---	---	---	---	---	---

0	1	1	0	1	0	0	1
---	---	---	---	---	---	---	---

**signal** u: row;

**signal** v: array1;

u(0) <= v(1)(2);

# User Defined Array Data Type

**type array2 is array (0 to 3) of std\_logic\_vector(7 downto 0);**

- Define a **1D × 1D array** named as **array2** with 4 rows of vectors (eight STD\_LOGIC values)
- Same as array 1

**type array3 is array (0 to 3, 7 downto 0) of std\_logic;**

- Define a **2D array** named as **array3** with an array of (4, 8) STD\_LOGIC values

0	1	1	0	1	0	0	1
0	1	1	0	1	0	0	1
0	1	1	0	1	0	0	1
0	1	1	0	1	0	0	1

# User Defined Array Data Type

**type** row **is** array (7 downto 0) **of** std\_logic;

**type** array1 **is** array (0 to 3) **of** row;

**type** array3 **is** array (0 to 3, 7 downto 0) **of** std\_logic;

**signal** u: row;

**signal** v: array1;

**signal** x: array3;

u(0) <= v(1)(2);

u(2) <= x(2, 1);



# Record Data Type

- Group a number of common signals together to simplify the port list in the entity

- e.g., **type** `my_record` **is record**

`rx: std_logic;`

`cts: bit;`

`tx: std_logic;`

**end record;**

**signal** `one_record: my_record;`


`one_record.tx <= '1';`

`one_record <= (rx => '1', cts => '1', tx => '1');`

# Exercise

Declare a record type that consists of an 8 bit\_vector, an 8-bit integer and a time type

# VHDL Format and Synthax

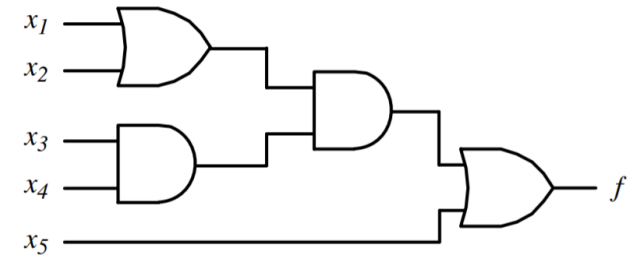

Library declaration	<pre>library IEEE; use IEEE.std_logic_1164.all;</pre>	<pre>-- load to access a library -- Use a package in the library.</pre>
Entity declaration	<pre>entity logic_c is     port (x1, x2, x3, x4, x5 : in bit;           f: out bit); end logic_c;</pre>	<pre>-- define the name of the entity -- inputs and data type -- outputs and data type</pre>
Architecture declaration	<pre>architecture behavior of logic_c is begin     f &lt;= ((x1 or x2) and           (x3 and x4)) or x5); end behavior;</pre>	<pre>-- define the architecture and -- specify the entity --define the logic operation</pre>

# Architecture

**Architecture declaration:** describes the logic function of the corresponding entity.

The most basic structure of an architecture


```
architecture arc_name of entity_name is
begin
    functional code
end arc_name;
```

# 4.4 VHDL Operators

## Operators for BIT and BOOLEAN types

Logical operation	Operator	Example
AND	AND	Z <= A AND B;
NAND	NAND	Z <= A NAND B;
NOR	NOR	Z <= A NOR B;
NOT	NOT	Z <= NOT (A);
OR	OR	Z <= A OR B;
XNOR	XNOR	Z <= A XNOR B;
XOR	XOR	Z <= A XOR B;

# Example

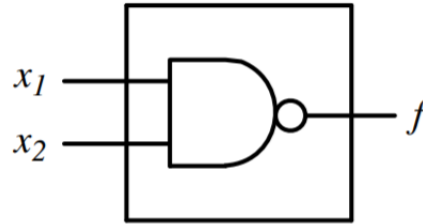

**architecture Behavior of nand\_gate is  
begin**

```
f <= not (x1 and x2);
```

**end Behavior;**

Alternative:

```
f <= x1 nand x2;
```

# Concatenation Operator (&)

To combine two bits or bit vectors

e.g.

A1 = "0000"   A2 = "10"   A3 = '0'   A4 = '1'

A1 & A2 = "000010"

A1 & A3 = "00000"

A2 & A3 = "100"

etc...

# Arithmetic Operators

## Operators for numeric types

Arithmetic operation	Operator	Example
Addition	+	<code>Z &lt;= A + B;</code>
Subtraction	-	<code>Z &lt;= A - B;</code>
Multiplication	*	<code>Z &lt;= A * B;</code>
Division	/	<code>Z &lt;= A / B;</code>
Exponentiating	**	<code>Z &lt;= 4 ** 2; (4<sup>2</sup>)</code>
Modulus	MOD	<code>Z &lt;= A MOD B;</code>
Remainder	REM	<code>Z &lt;= A REM B;</code>
Absolute value $ \pm A  = A$	ABS	<code>Z &lt;= ABS A;</code>



# REM vs MOD (FYI)

## Remainder: Same as mathematical operation

5 rem 3 = 2 -- 5/3 remainder is 2

(-5) rem 3 = -2

5 rem (-3) = 2

(-5) rem (-3) = -2

$$\begin{array}{r} 1 \\ 3 \overline{) 5} \\ \underline{3} \\ 2 \end{array}$$

$$\begin{array}{r} -1 \\ 3 \overline{) -5} \\ \underline{-3} \\ -2 \end{array}$$

$$\begin{array}{r} -1 \\ -3 \overline{) 5} \\ \underline{3} \\ 2 \end{array}$$

$$\begin{array}{r} 1 \\ -3 \overline{) -5} \\ \underline{-3} \\ -2 \end{array}$$

# REM vs MOD (FYI)

## Modulus:

- (1)  $(A \bmod B)$  has the sign of  $B$
- (2)  $(A \bmod B)$  has an absolute value smaller than the absolute value of  $B$
- (3)  $(A \bmod B) = A - B * N$  with  $A$ ,  $B$  and  $N$  are integers

$$5 \bmod 3 = 2$$

$$-- 5 - (3 * 1) = 2$$

$$(-5) \bmod 3 = 1$$

$$-- -5 - (3 * -2) = 1$$

$$5 \bmod (-3) = -1$$

$$-- 5 - (-3 * -2) = -1$$


$$(-5) \bmod (-3) = -2$$

$$-- -5 - (-3 * 1) = -2$$

# REM vs MOD (FYI)


**Modulus: Think of a clock!**

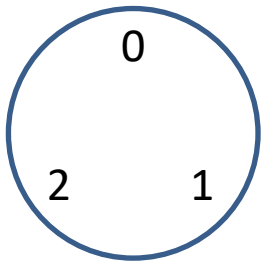- (1) For  $(A \bmod B)$ , A clock that count from 0 to  $\text{abs}(B)-1$
- (2)  $AB$  is pos  $\rightarrow$  clockwise for A steps starting from 0
- (3)  $AB$  is neg  $\rightarrow$  anticlockwise for A steps starting from 0
- (4) Sign of  $(A \bmod B)$  follows B




$5 \bmod 3$

2

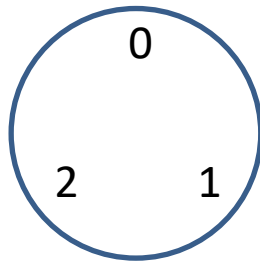


$-5 \bmod 3$

1

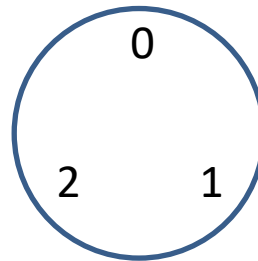

$5 \bmod -3$

-1

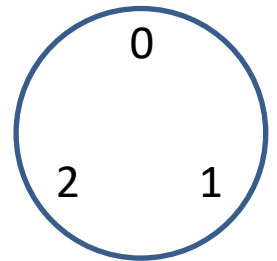

$-5 \bmod -3$

-2

# REM vs MOD (FYI)

Work out the following

$M \leq \text{index mod } 4;$

Index	-9	-8	-7	-6	-5	-4	-3	-2	-1	0	1	2	3	4	5	6	7	8	9
M																			

$M \leq \text{index rem } 4;$

Index	-9	-8	-7	-6	-5	-4	-3	-2	-1	0	1	2	3	4	5	6	7	8	9
M																			

# Relational Operators

Relational operation	Operator	Example
Equal to	=	If (A = B) Then
Not equal to	/=	If (A /= B) Then
Less than	<	If (A < B) Then
Less than or equal to	<=	If (A <= B) Then
Greater than	>	If (A > B) Then
Greater than or equal to	>=	If (A >= B) Then

Use for comparison

# Shift Operators (Logical)

Shift operation	Operator	Remark
Shift Left Logical	sll	Shift left and fill blank with 0
Shift Right Logical	srl	Shift right and fill blank with 0
Rotate Left Logical	rol	Circular operation
Rotate Right Logical	ror	Circular operation
Shift Left Arithmetic	sla	Shift left and fill blank with LSB
Shift Right Arithmetic	sra	Shift right and fill blank with MSB

A1 = "1011"

1) A1 sll 1    -- 0110

2) A1 sll 3    -- 0110 then 1100 then 1000

3) A1 sll -3    -- A1 srl 3

# Shift Operators (Logical)

Operator	Remark
sll	Shift left and fill blank with 0
srl	Shift right and fill blank with 0
rol	Circular operation
ror	Circular operation
sla	Shift left and fill blank with LSB
sra	Shift right and fill blank with MSB

A1 = "1011"

1) A1 sll 1 -- 0110

2) A1 sll 3 -- 0110 then 1100 then 1000

3) A1 sll -3 -- A1 srl 3

4) A1 srl 3 -- 0101 then 0010 then 0001

5) A1 sla 3 -- 0111 then 1111 then 1111

6) A1 sra 3 -- 1101 then 1110 then 1111

7) A1 rol 3 -- 0111 then 1110 then 1101

8) A1 ror 3 -- 1101 then 1110 then 0111

# Precedence of VHDL Operators

Precedence (High to Low)	Operators
1	** abs NOT
2 Multiplying	* / mod rem
3 Unary (Sign)	+ -
4 Adding	+ - &
5 Shift	sll srl sla sra rol ror
6 Relational	= /= < <= > >=
7 Logic	and or nand nor xor xnor

- Operators in the same class are applied from left to right
- Parentheses change the order of precedence; and good coding style



# Exercise

Transform the following logic expression to VHDL code

1)  $f = ab' + a'b$

2)  $f = a(b' + a')b$


# Exercise

Transform the following logic expression to VHDL code

Boolean	VHDL Boolean
$Y = \overline{AB}$	
$Y = \overline{A + B}$	
$Y = A + BC$	
$Y = C\overline{X} + \overline{D}$	
$Y = A\overline{B}C + \overline{A}\overline{B}C + \overline{A}B\overline{C}$	

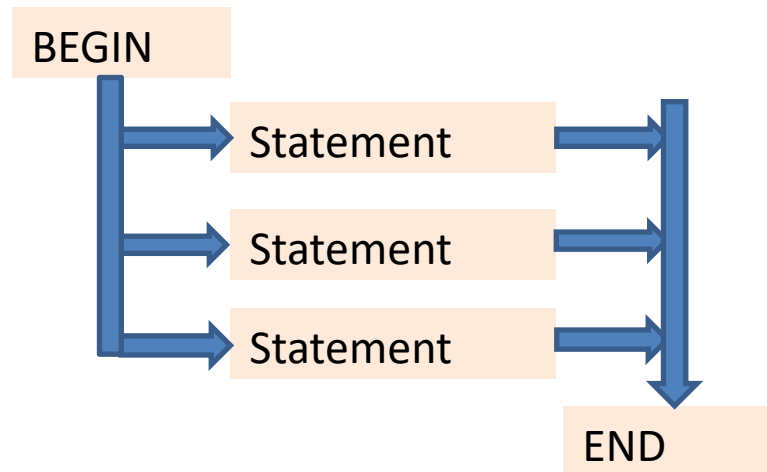
# 4.5 VHDL Synthax for Logic Circuits

- VHDL code describes the circuit **design with Boolean expressions**
- It is different from a computer program which is composed of a **sequence** of instructions for the CPU to execute
- VHDL Boolean expressions are statements only used for configuring the FPGA chip (no CPU to execute these statements )



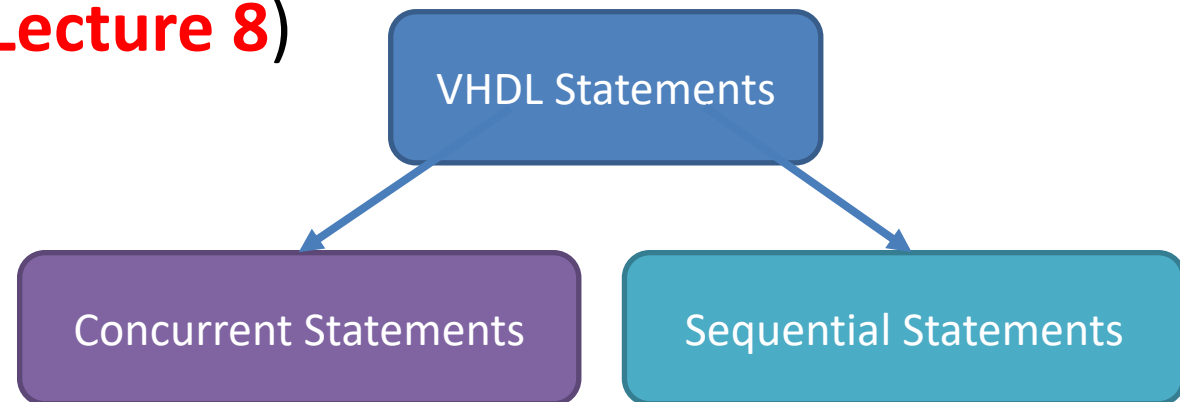
# Concurrent vs Sequential Statements

- VHDL models **combinational circuit** using **concurrent statements**
- **Concurrent statements**: All statements written in the **architecture** body will be executed **concurrently** (not in sequence!)
- **Sequential statements**: Statements within a **process** in the architecture body are executed **sequentially** (will be discussed in **Lecture 8**)



# Example

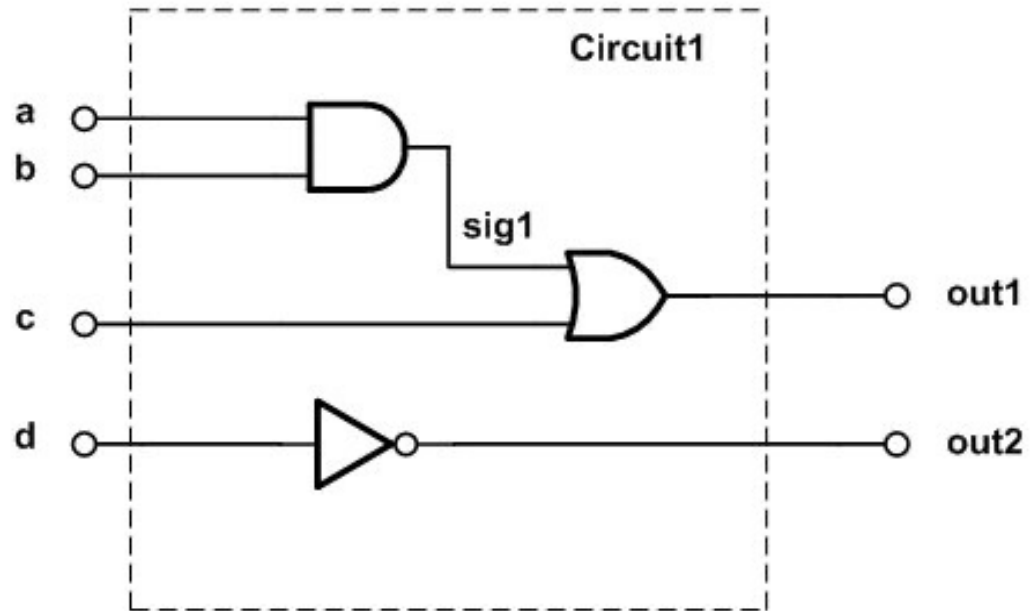

Precedence order is NOT important for concurrent statements !!


```
sig1 <= (a and b);  
out1 <= (sig1 or c);  
out2 <= (not d);
```

=

```
out1 <= (sig1 or c);  
sig1 <= (a and b);  
out2 <= (not d);
```

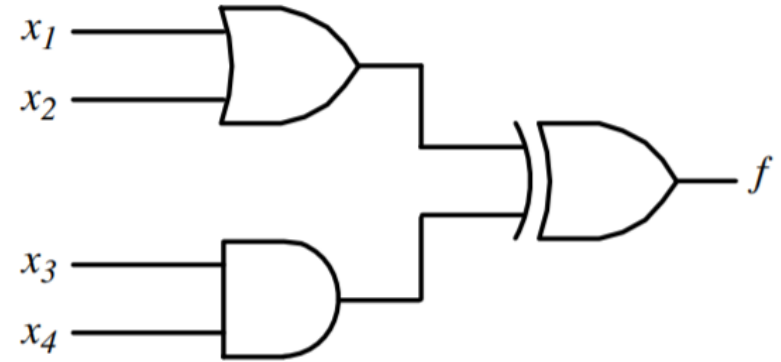
# Exercise

Write your own VHDL statement to describe the logic circuit


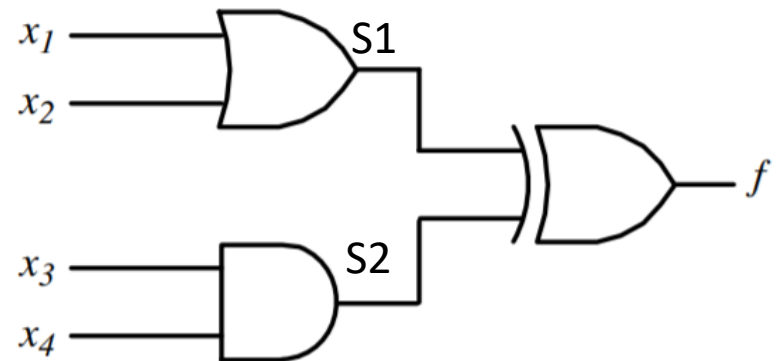
# Example of Complete Module

```
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity logic_c is  
    port (x1, x2, x3, x4 : in bit;  
          f: out bit);  
end logic_c;  
  
architecture behavior of logic_c is  
    signal S1, S2 : bit;  
begin  
    S1 <= x1 OR x2;  
    S2 <= x3 AND x4;  
    F <= S1 XOR S2;  
end behavior;
```



# Exercise

Write your own VHDL statement to describe the logic circuit

